

Mastering Digital Design

with Verilog on FPGAs

John Wickerson

Lecture 1

Module aims


- To ensure that all MSc students reach a **common competence level** in RTL design using FPGAs in a hardware description language.
- To act as a **revision exercise** for those already competent in Verilog and FPGAs.

Format


- The lab experiment is divided into four parts.
- It is hoped that you will finish one part each week.
- Each part has clearly defined Learning Outcomes.
- These lectures will supplement the lab with some background information.

Grading

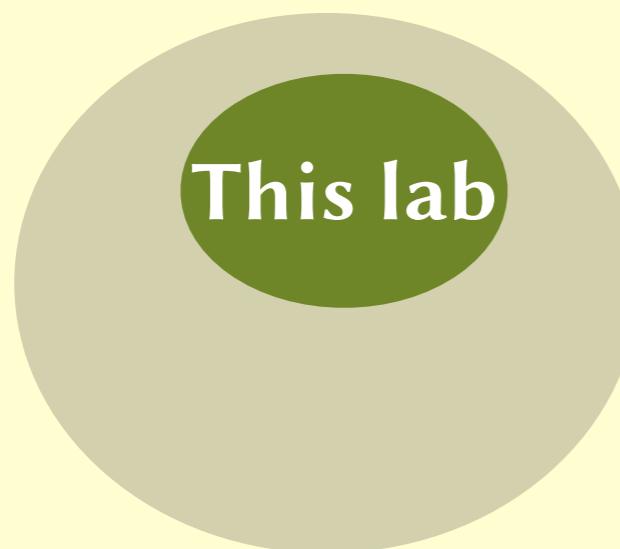
- This lab is part of the Coursework component of the MSc course.
- You must pass this component, but it does not count towards your final MSc grade.



Coursework

 

Exams

 


Project

Assessment

- Assessment will be via a 15-minute **oral interview**. This will assess:
 - how many parts of the experiment you have completed,
 - the extent to which you have understood the underlying principles of digital design, and
 - whether you have used a logbook (electronic or paper) to help you learn through planning and reflection.
- Please have your equipment set up and ready to demo.

Admin

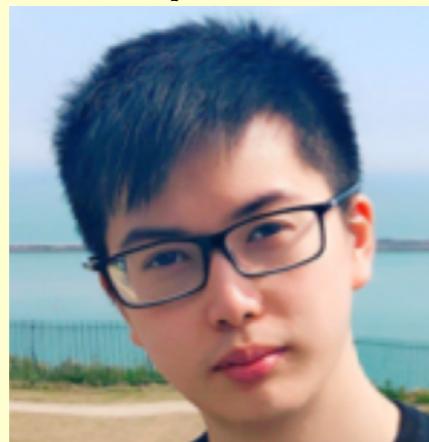- **Lectures:** Fridays at 1400–1600, starting today, for 4 weeks.
- **Labs:** Tuesdays at 0900–1200, starting 19th October, for 4 weeks.
- **Teaching assistants:**
Mr Jianyi Cheng and Mr Diederik Vink.



- **Course webpage:**
https://github.com/johnwickerson/mastering_digital_design

Supporting mixed-mode

- The software you need is installed on the machines in the MSc computer room, but it's not covid-friendly for you to all pile in there simultaneously.
- If you own a Linux/Windows machine, you can install Quartus Lite 20.1 natively though from the Intel website (<https://fpgasoftware.intel.com/?edition=lite>). You may have to create a (free) account to download Quartus. When installing it, choose Cyclone V device support, which is needed for the DE1 SoC board.
- A virtual machine has been set up, with Quartus Lite and device support ready-installed. All users, including Mac users, can use this VM to program the FPGA. The VM is available from Box (<https://imperialcollegelondon.box.com/s/btnnde421v5m3amq0t98zqfab5njhvza3>). See the README.txt therein for setup instructions.
- The lectures will be entirely on Teams; the labs will be mainly on Teams.

To do

1. Group yourselves into pairs.
2. Tell me who is in your pair.
3. Collect a DE1-SoC board from Stores (Level 1), one per pair.
You'll need to have your college card with you.
4. Do the exercises, with support from the GTAs on Tuesday mornings, and keep a logbook along the way.
5. Turn up to your 15-minute viva (with your logbook) near the end of this term.

Credits

- This course was conceived and designed by **Professor Peter Cheung.**





- Any errors in the lectures or the labs are mine. (And please do let me know if you find any!)

Digital Design


The old days

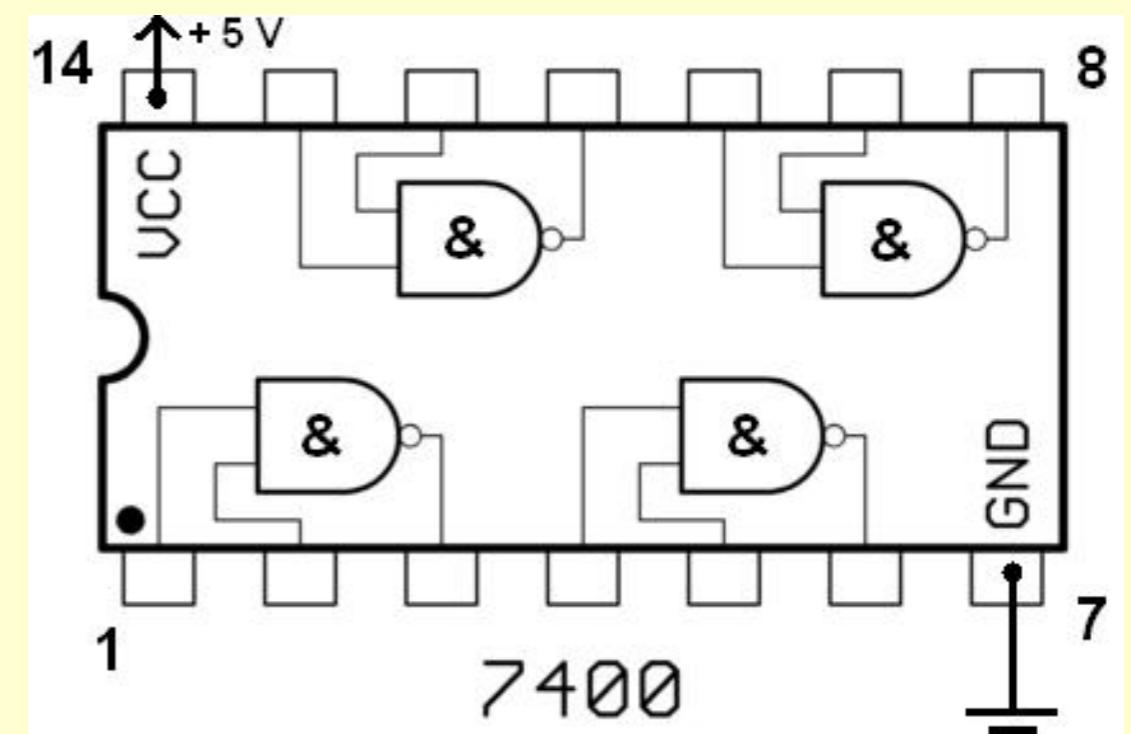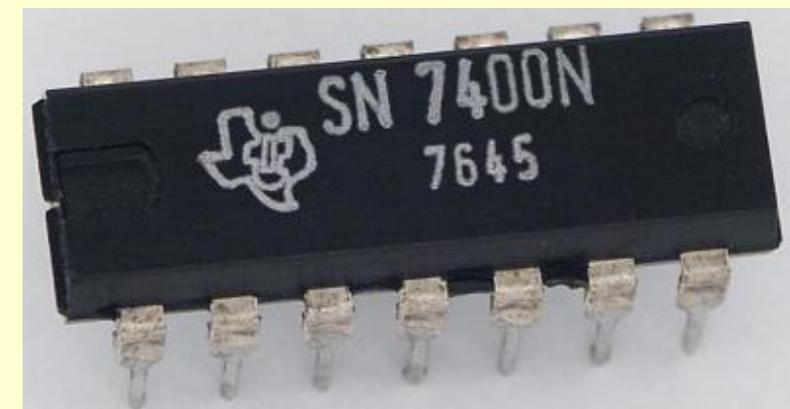- **Discrete logic**, built from individual gates or packages containing small digital building blocks (e.g. a 1-bit adder).
- Thanks to De Morgan, we can build *anything* using 2-input NAND gates!
- But this is tedious, expensive, and prone to wiring errors.




Early integrated circuits

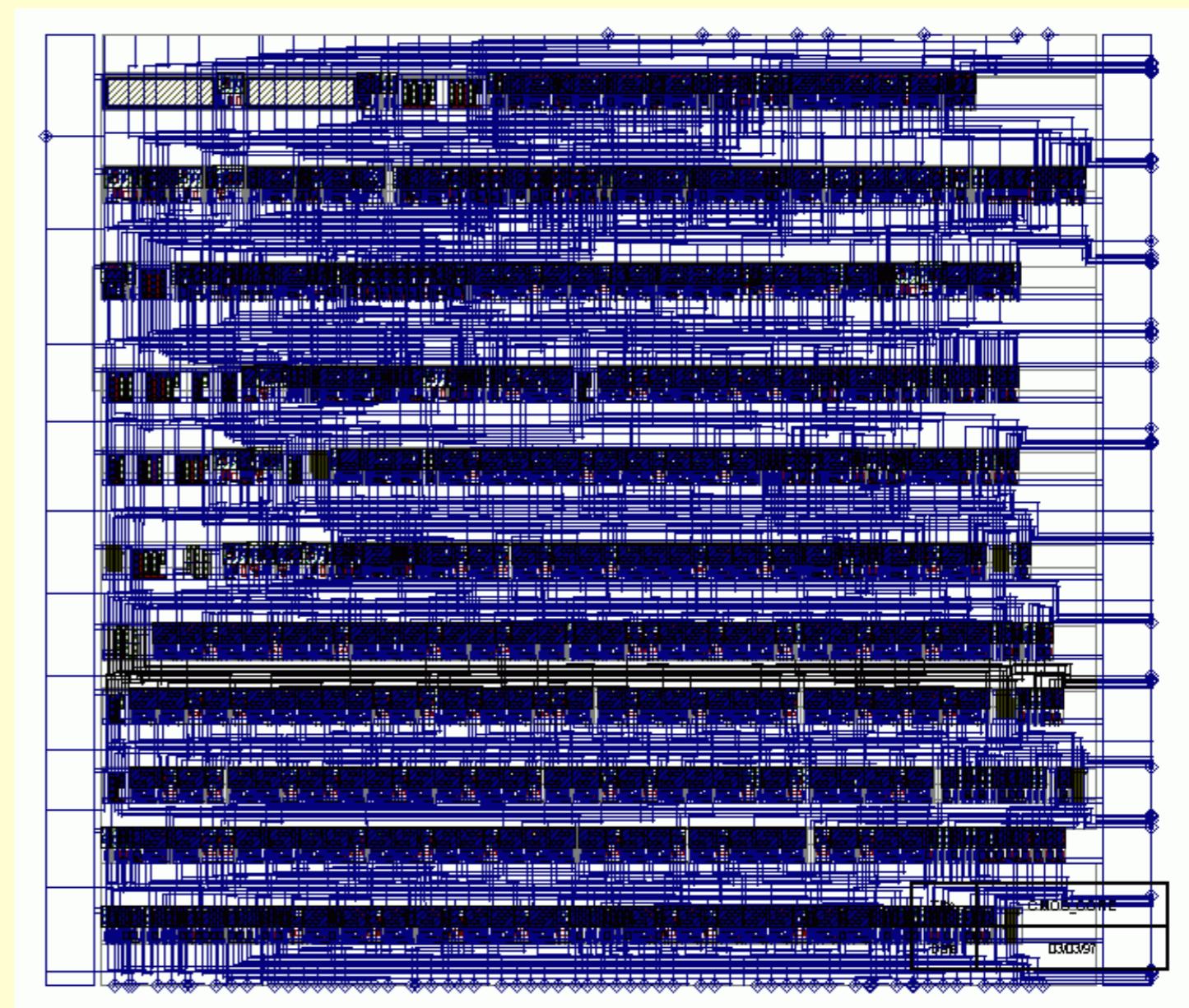- Rows of gates, connected to form **application-specific integrated circuits** (ASICs).
- Can be **full-custom** (fabricated from scratch), or **semi-custom** (can only adjust the wiring between rows).
- Functionality cannot be later changed.



Full-custom ICs

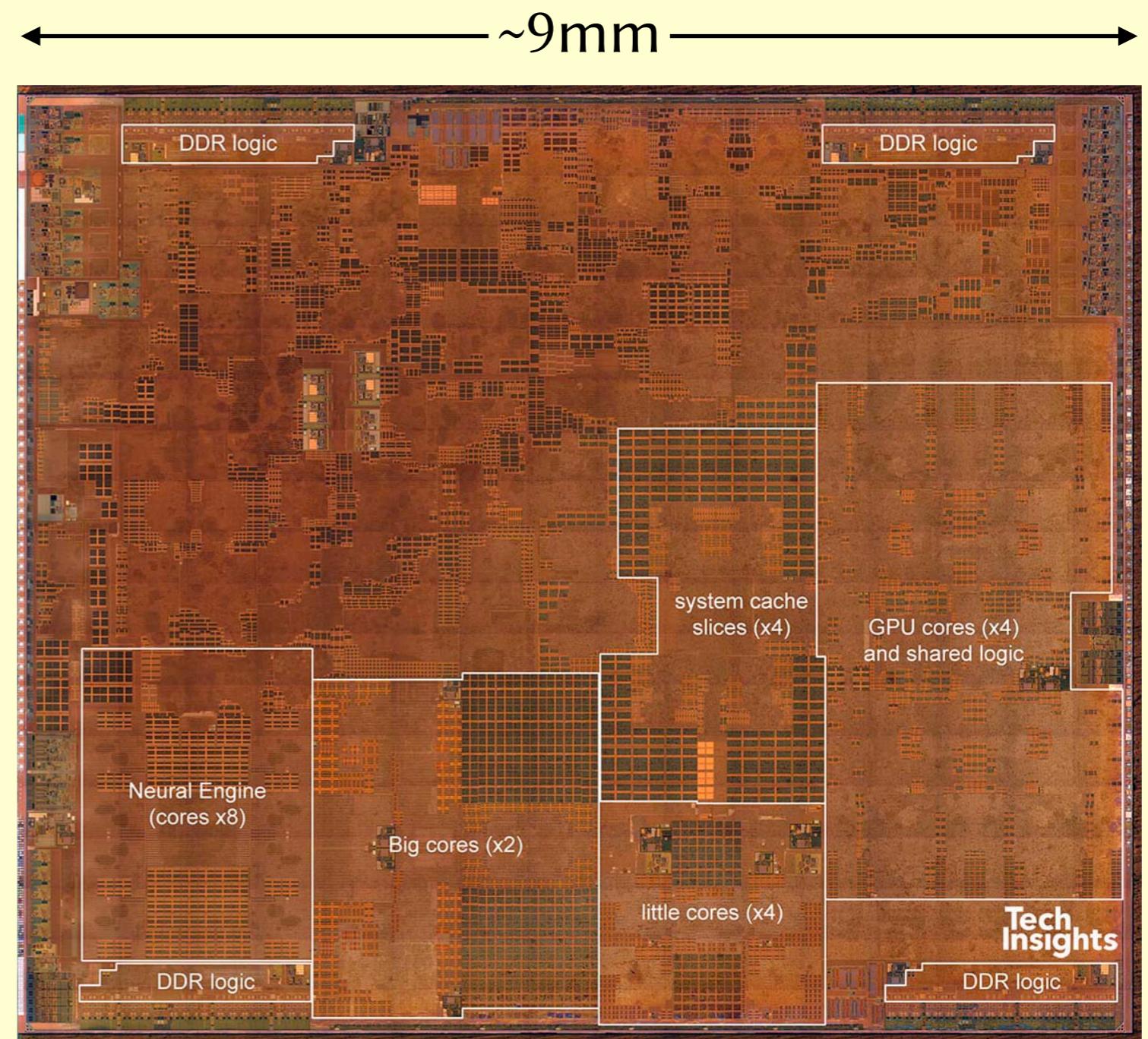
- Here is an **Apple A12** processor from the **iPhone XS**. It has about 6.9 billion transistors.
- Very expensive to design and manufacture, so not viable unless the market is very large.



<https://www.techinsights.com/blog/apple-iphone-xs-max-teardown>


Field-programmable gate arrays (FPGAs)

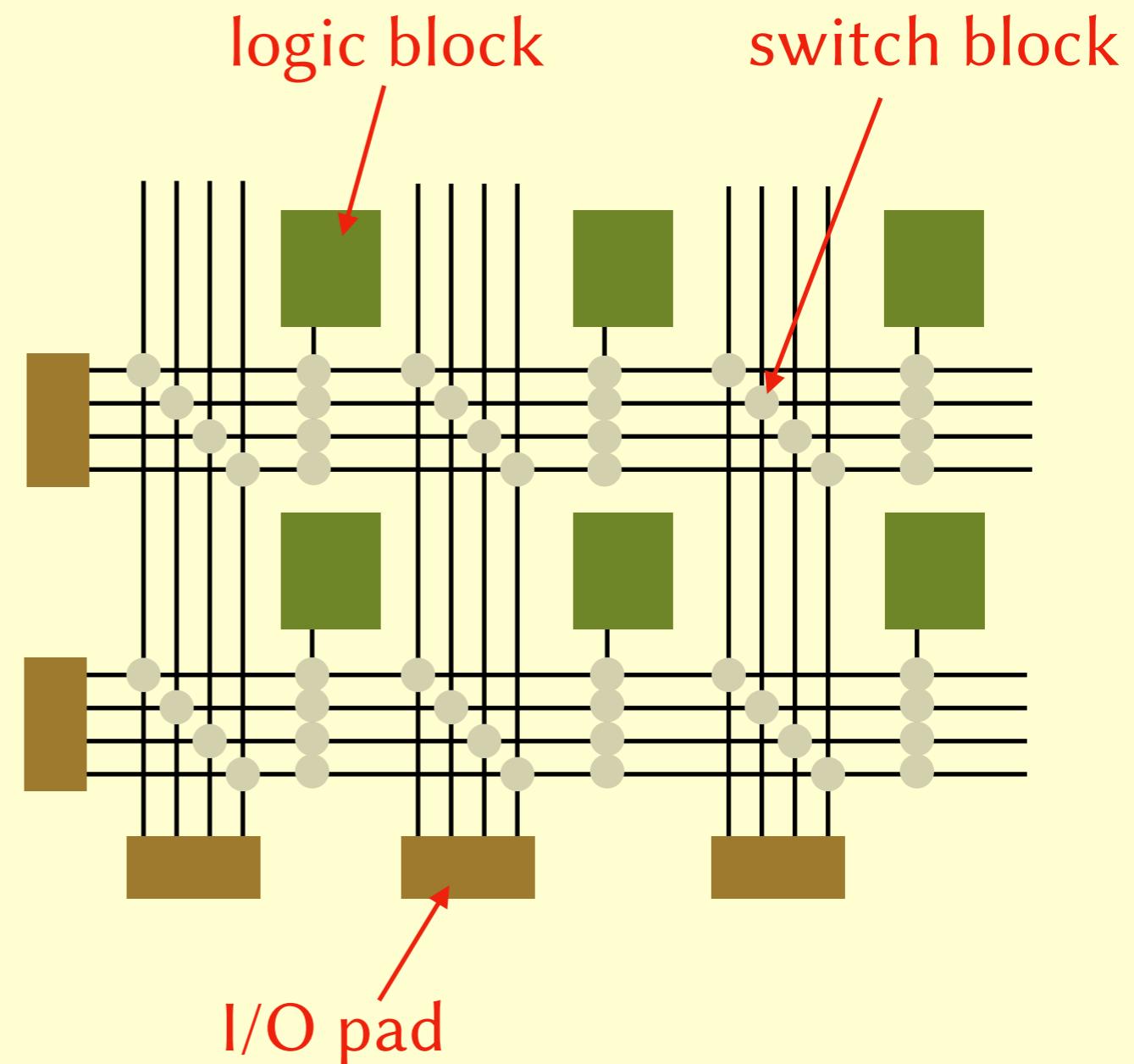- Introduced by **Xilinx** in 1985. Other manufacturers include **Altera** (now part of **Intel**), **Microsemi** (now part of **Microchip**), and **Lattice**.
- Arrays of programmable logic blocks, programmable wiring in between, and flexible I/O.




Logic blocks

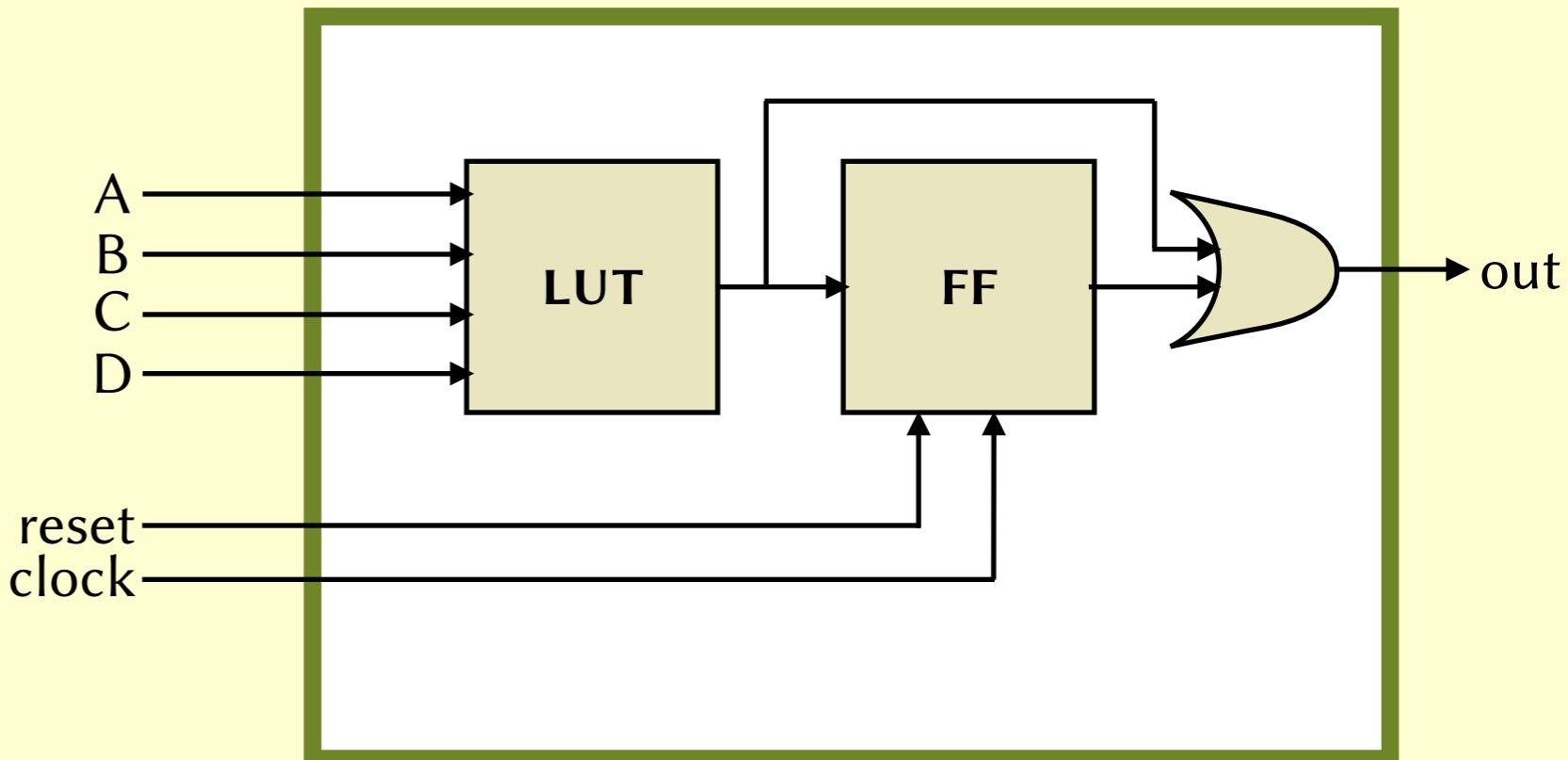- Also called *logic elements*.
- Based around **look-up tables** (LUTs), usually with 4 inputs.
- Optional flipflop (FF) at the output.
- These can implement *any* 4-input Boolean function (truth table).




Multiplexer (MUX)

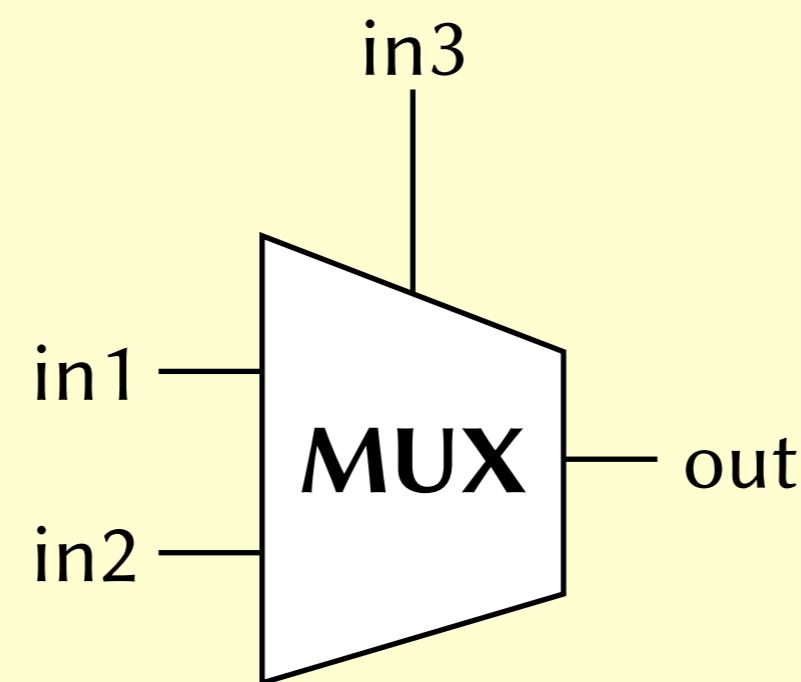


Logic blocks

| A | B | C | D | X |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |


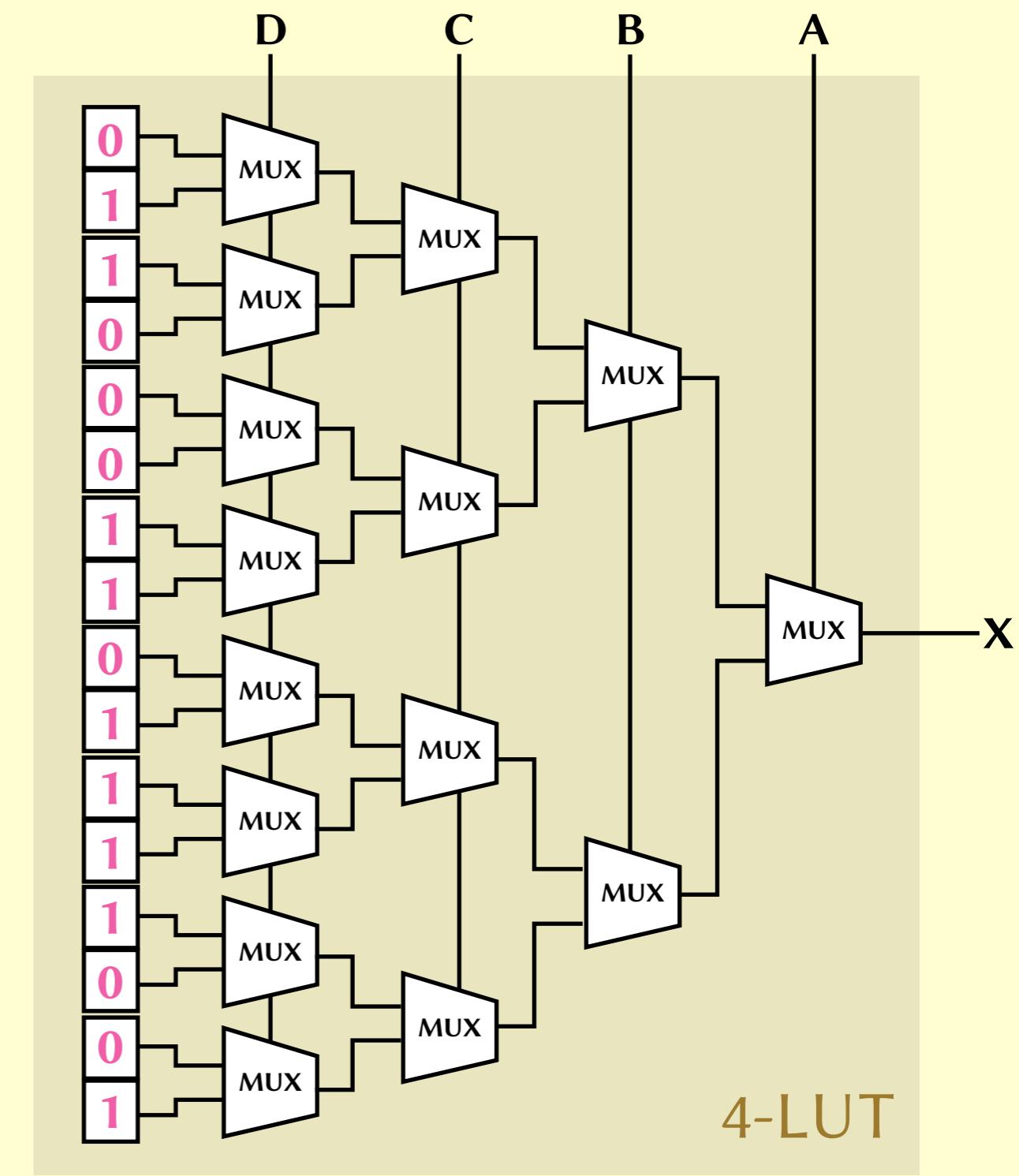


Field-programmable gate arrays (FPGAs)


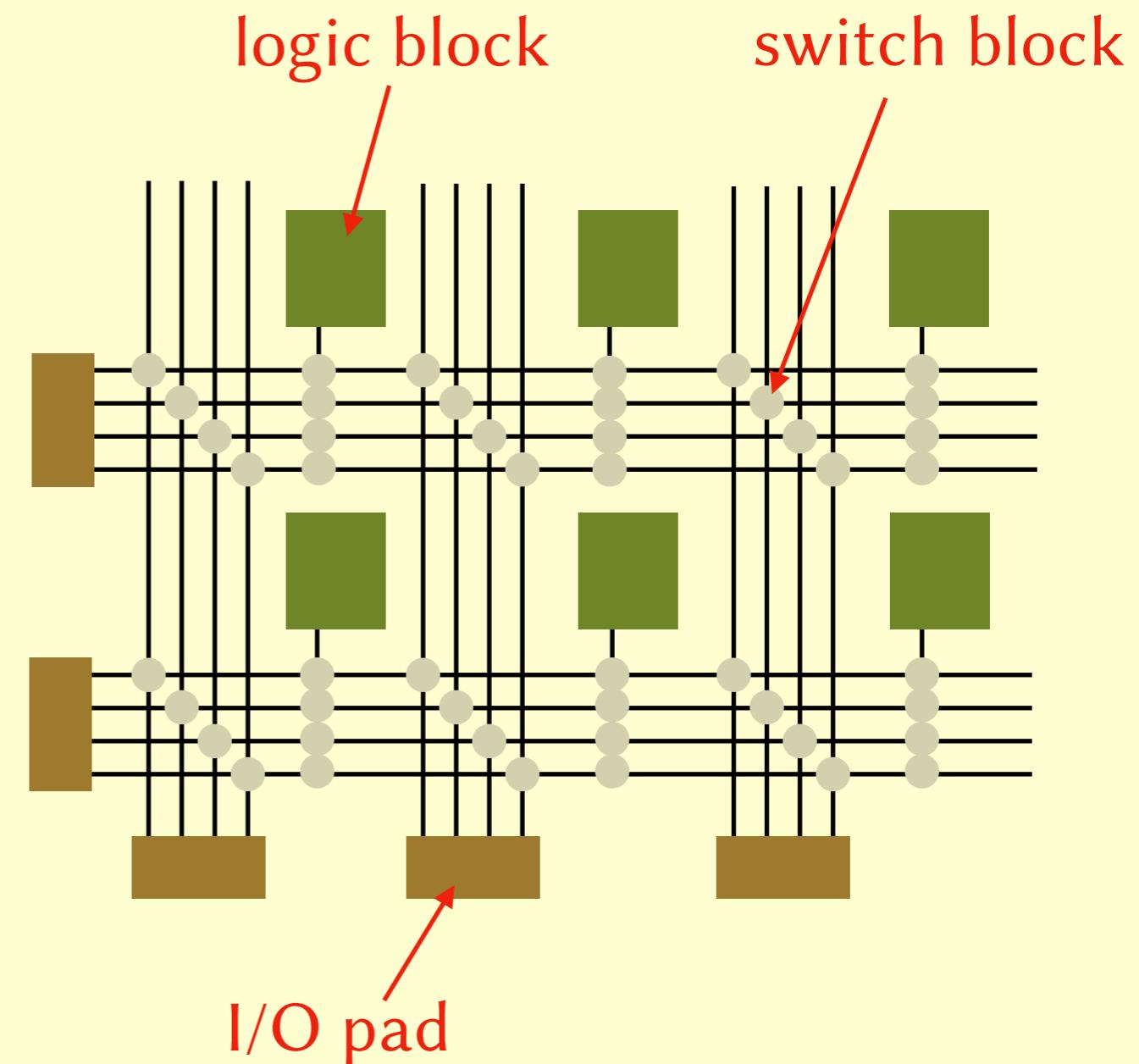
- Introduced by **Xilinx** in 1985. Other manufacturers include **Altera** (now part of **Intel**), **Microsemi** (now part of **Microchip**), and **Lattice**.
- Arrays of programmable logic blocks, programmable wiring in between, and flexible I/O.



Programmable routing

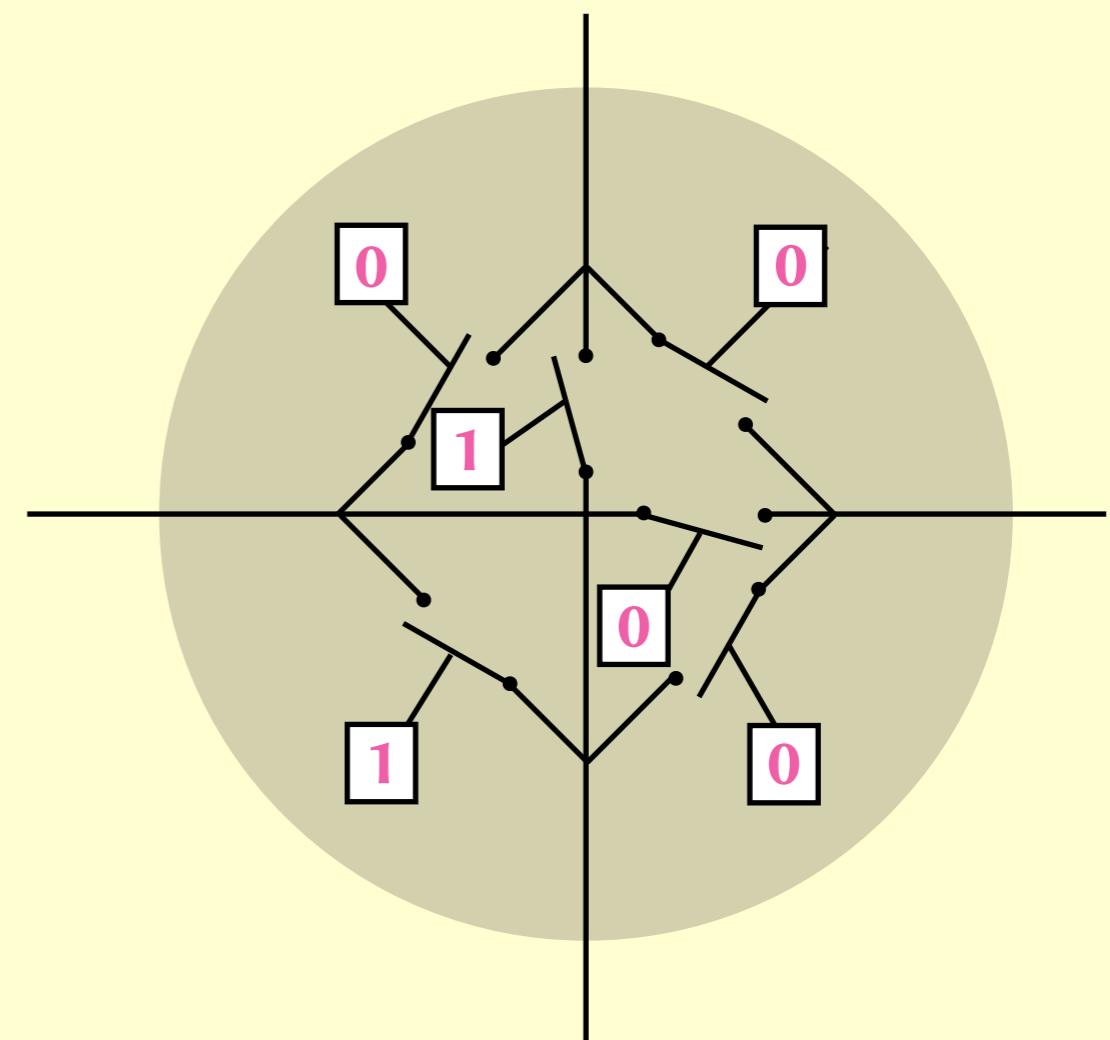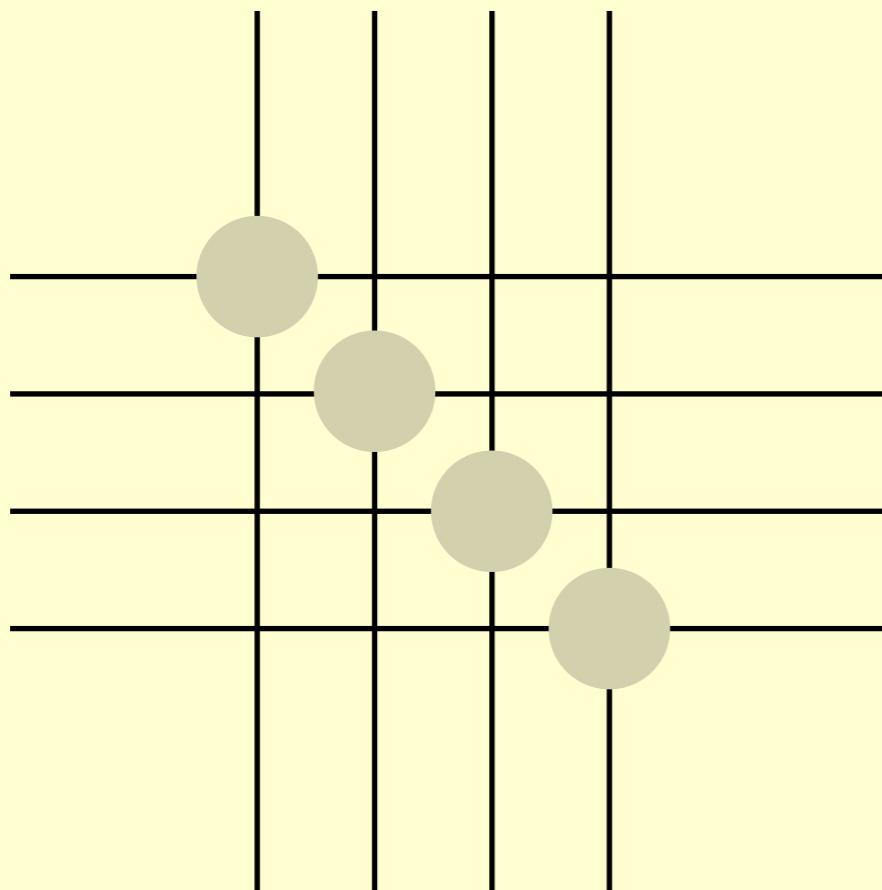

Programmable routing

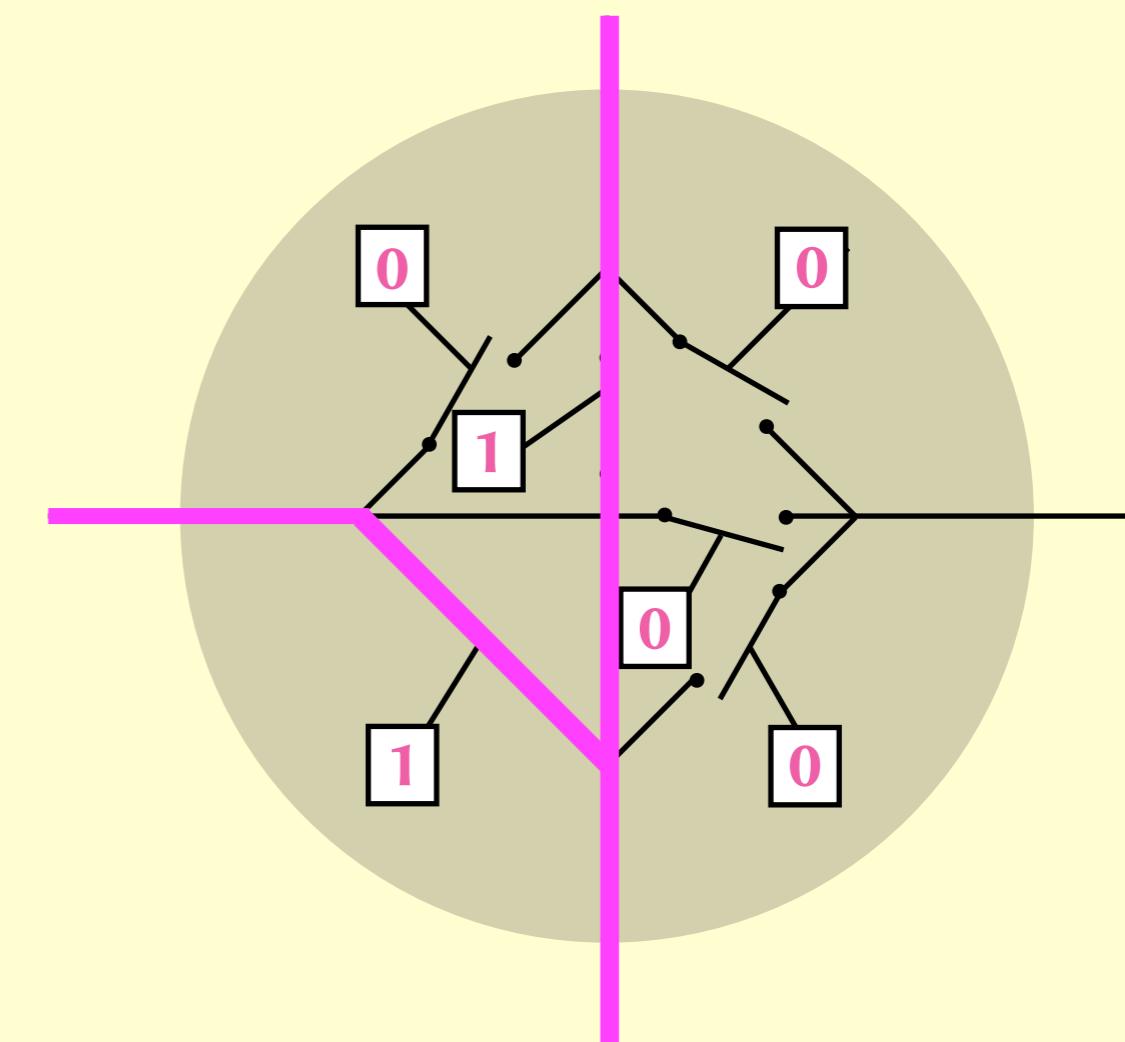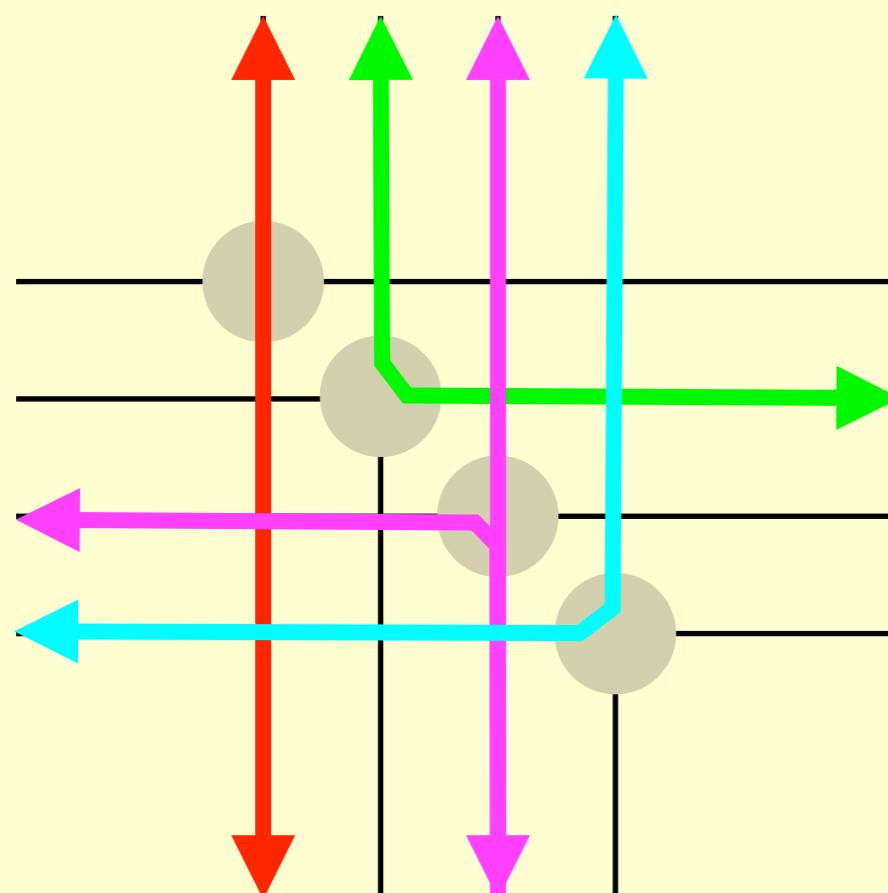


Configuring an FPGA

- All these configuration registers are set by passing the FPGA a **configuration bitstream**.
- Powering up the board puts the FPGA chip into a "waiting" mode (LEDs flashing). You then send the board the bitstream of your design via the USB port.


Cyclone V FPGA

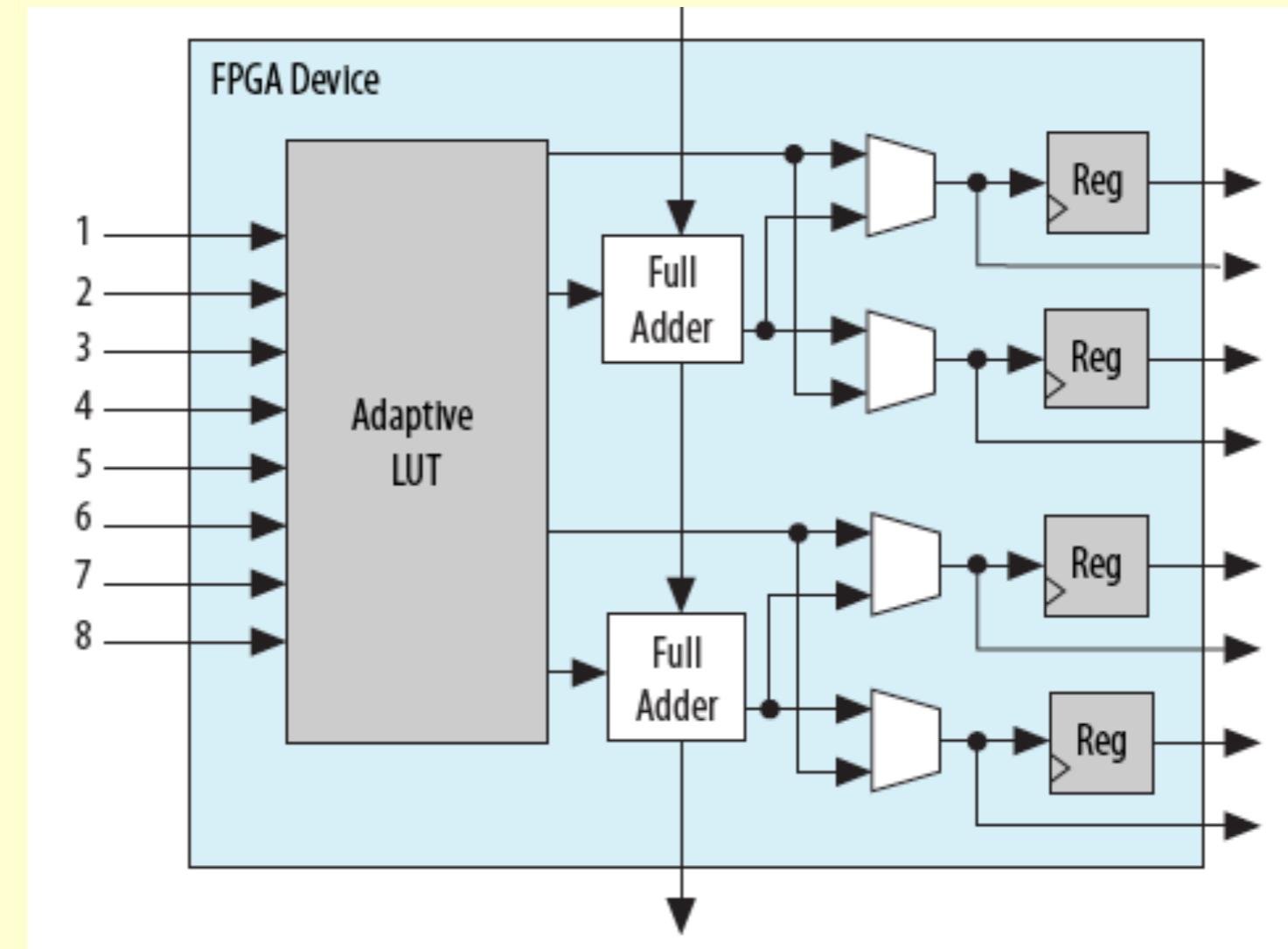- The Altera **Cyclone V** FPGA uses a more complex FPGA logic blocks called Adaptive Logic Modules (ALMs).
- The device we use (5CSEMA5F31C6N) has 32000 ALMs. That's roughly equivalent to 85000 4-LUTs, or about 2000 32-bit binary adders.
- Not that this particularly matters for FPGA *users*.




Cyclone V FPGA

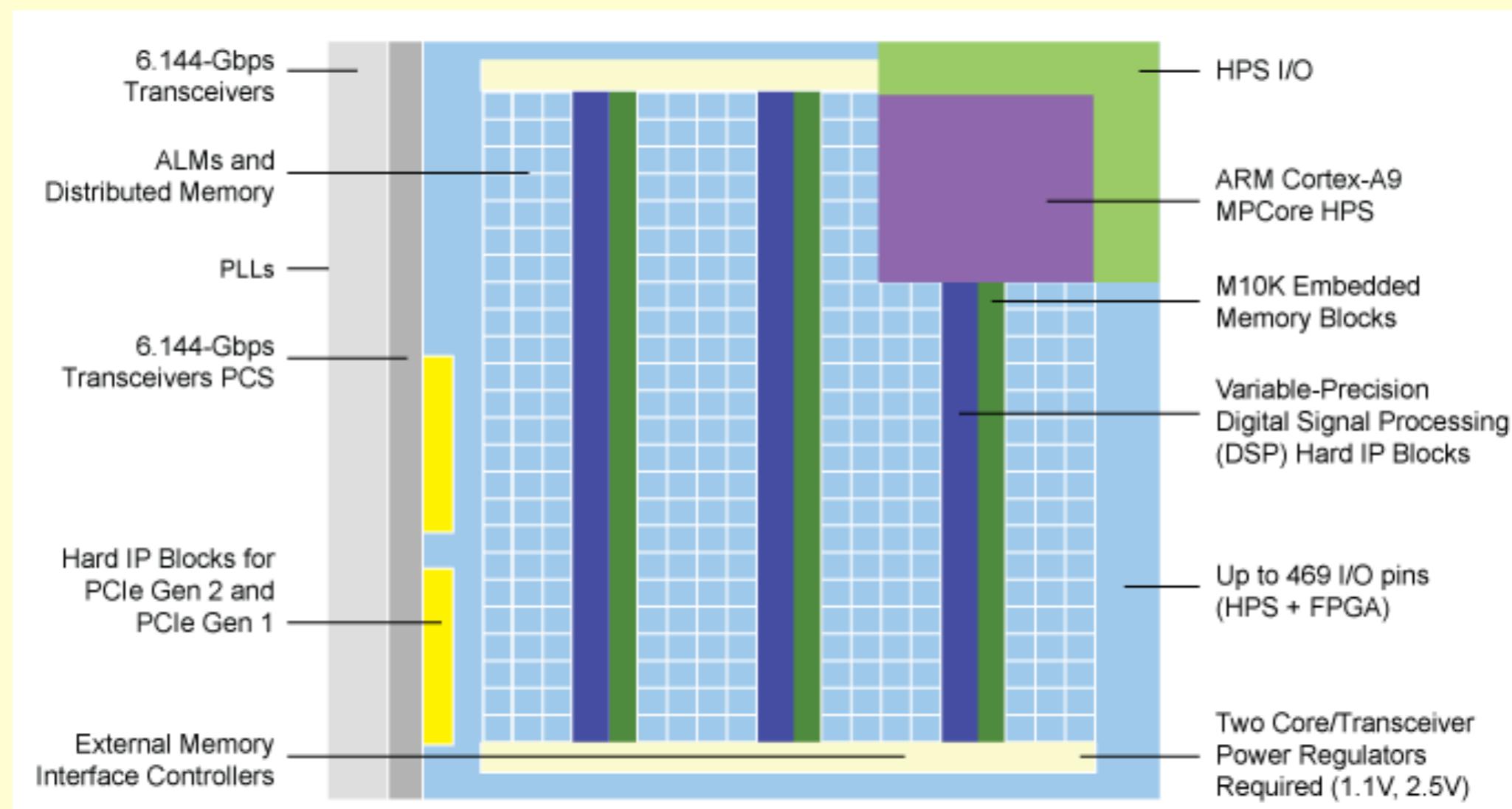- The Cyclone V also has 4MB of embedded memory, 87 DSP blocks (for multiply-accumulate), a 2-core ARM processor, and hard logic for interfacing with PCIe and external memory.





Design Tools

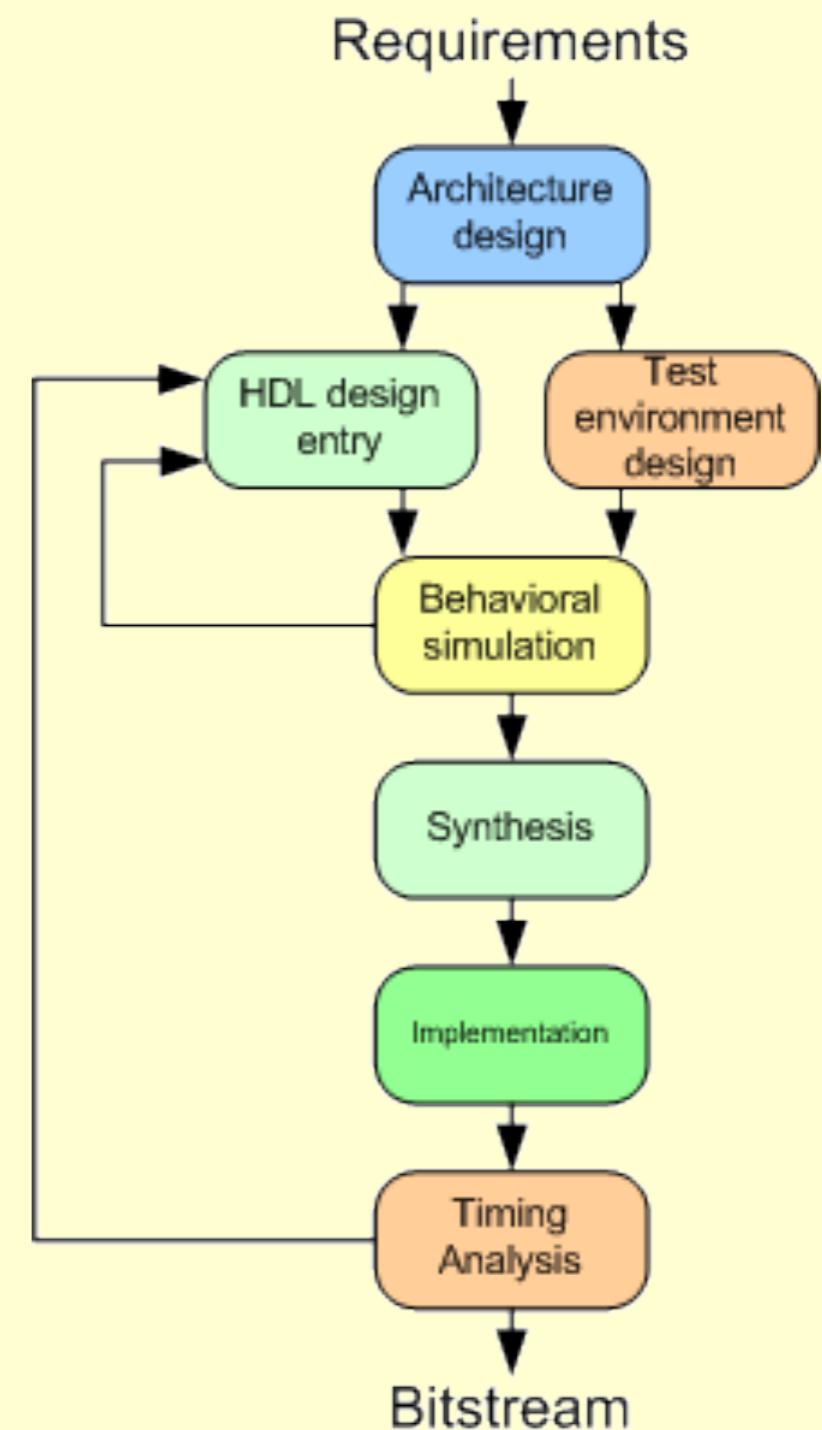- We use **Altera Quartus II** to design for FPGA.
- Features include: design entry, compilation from HDL, synthesis, simulation, timing analysis, power analysis, project management.
- The software is installed on all the PCs in the department, but this year we will also help you get it running on your own machine.





The DE1-SoC board

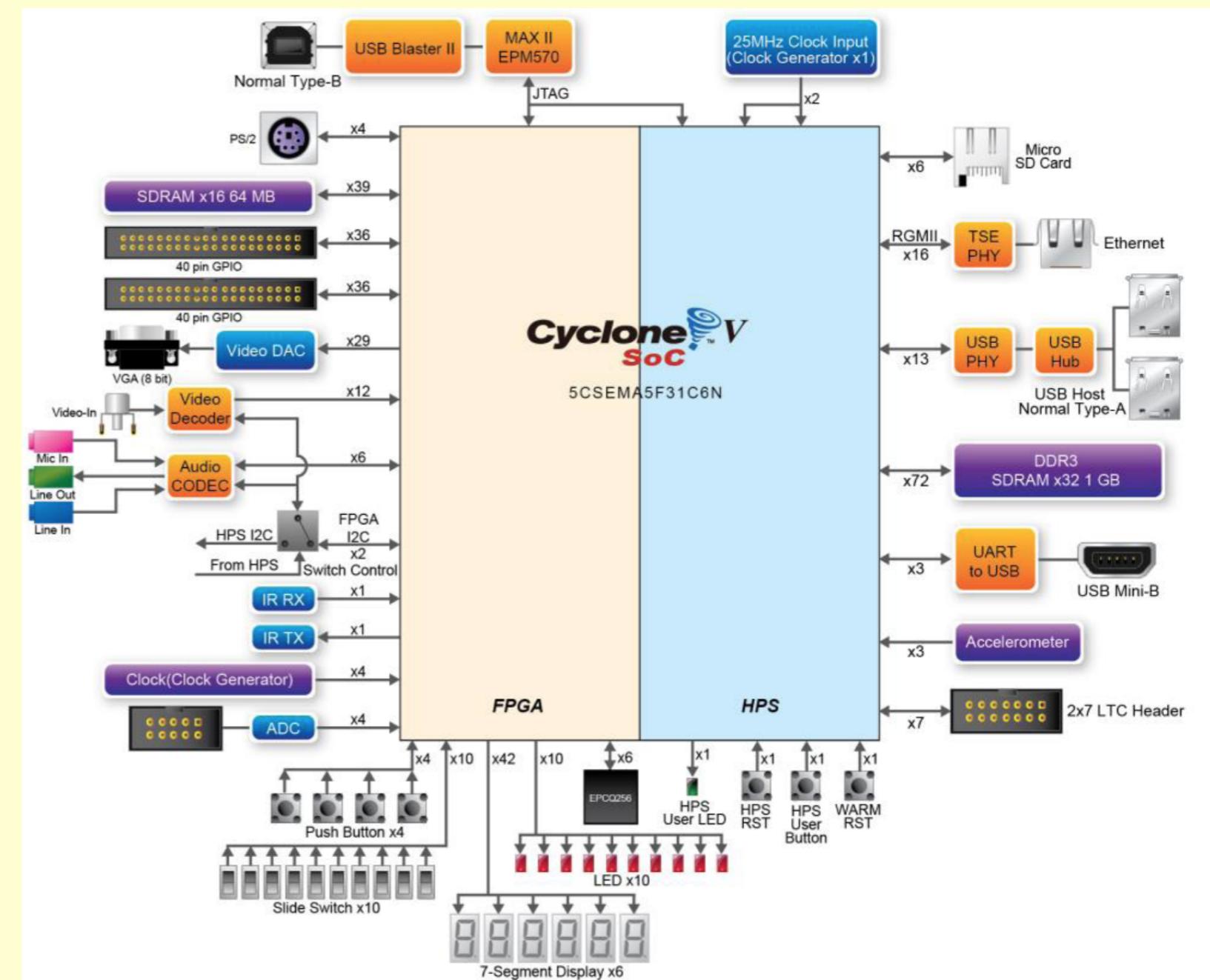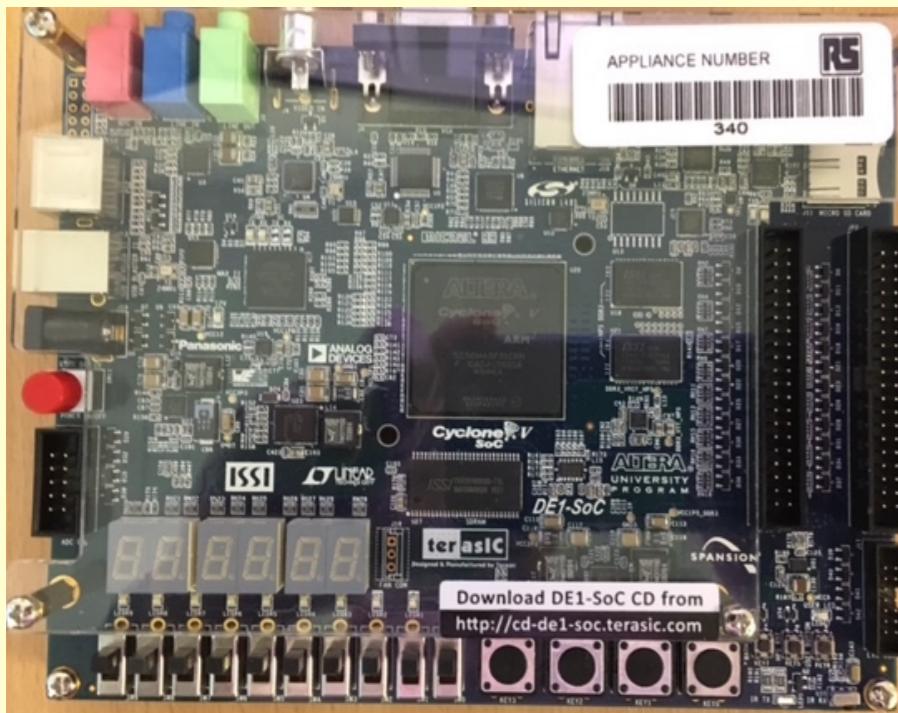- Everything you need to test basic designs involving switches, 7-segment displays, and even VGA output.



Add-on board

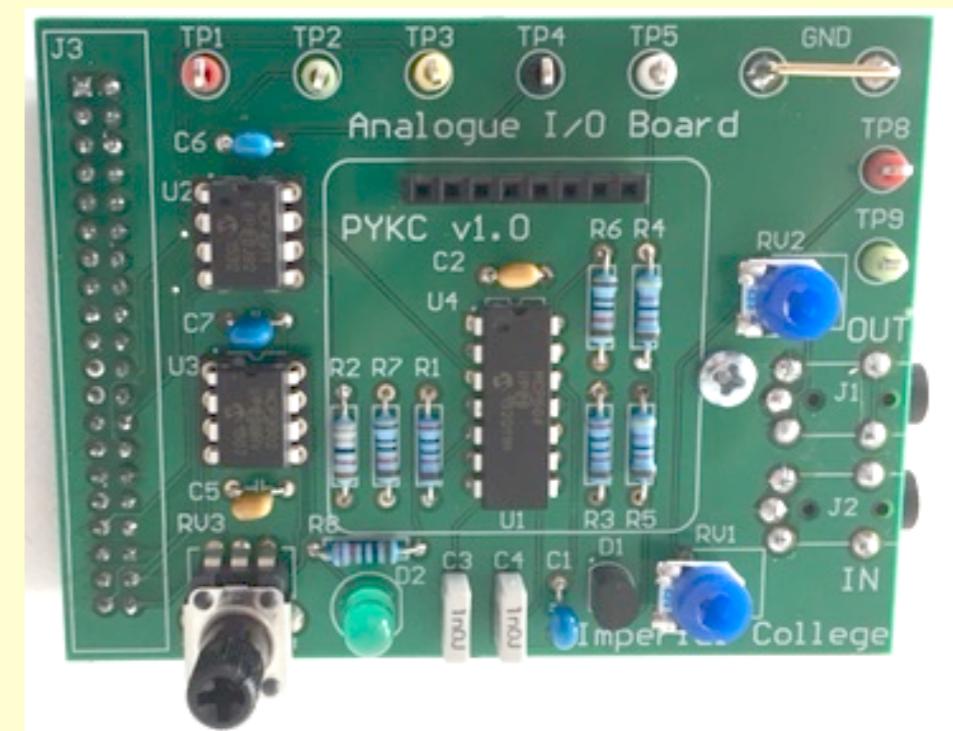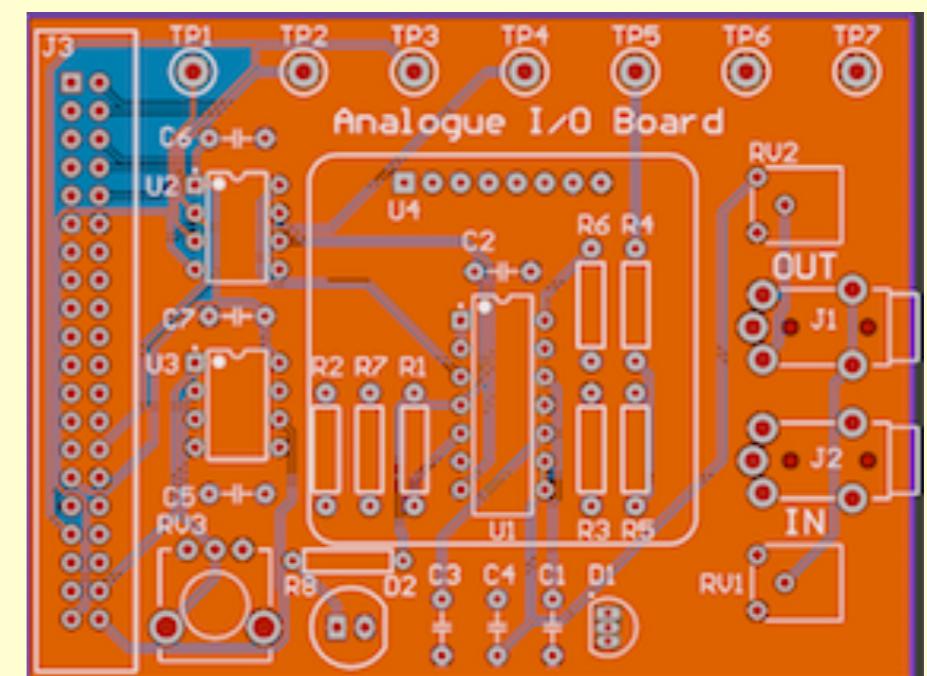- Provides analogue inputs (from microphone) and outputs (to headphone jack).
- Will feature in the third and fourth parts of the lab – you can ignore it for now.



Verilog

Verilog

- A **hardware description language** based on C syntax.
- Description can be at **behavioural level, register-transfer level (RTL), or gate level**.
- May be easier to learn than its competitor, VHDL. Other HDLs include Chisel and Bluespec.

Schematic vs HDL

Schematics:


- ✓ Provide overview
- ✓ Direct connection to hardware
- ✓ No programming needed

HDL:

- ✓ Flexible and parameterisable
- ✓ Simple textual format
- ✓ Connection to high-level languages

Verilog modules

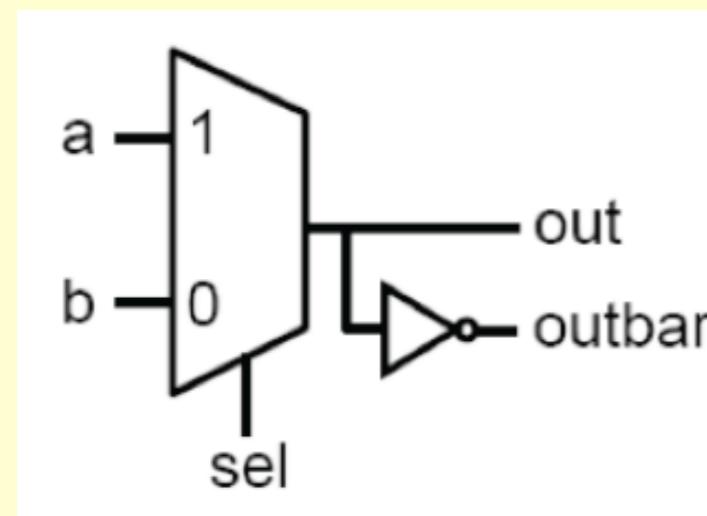- A Verilog design consists of many interconnected **modules**.
- A module contains low-level gates, statements, and other modules.



| a | b | sel | out | outbar |
|---|---|-----|-----|--------|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |

```
// Function: 2-to-1 multiplexer
module mux2to1 (out, outbar,
                  a, b, sel);
    output out, outbar;
    input a, b, sel;

    assign out = sel ? a : b;
    assign outbar = ~out;
endmodule
```

Verilog syntax

Specify port as **input**/
output/inout

Declare module,
list its ports,
terminate with ;

Comments can also
use /* ... */

Express module's behaviour.
Each statement executes in
parallel. Order doesn't matter.

This is continuous assignment.
Output responds to changes in
input **immediately**.

```
//Function: 2-to-1 multiplexer
module mux2to1 (out, outbar,
                  a, b, sel);
    output out, outbar;
    input a, b, sel;
    assign out = sel ? a : b;
    assign outbar = ~out;
endmodule
```


Other operators include: &, |, +, -, *

Gate-level description

- Built-in logic gates include: **and**, **nand**, **or**, **nor**, **xor**, **xnor**, **not**, **buf**.

```
// Function: 2-to-1 multiplexer as gates
module mux_gate (out, outbar,
                  a, b, sel);
  output out, outbar;
  input a, b, sel;
  wire out1, out2, selb;

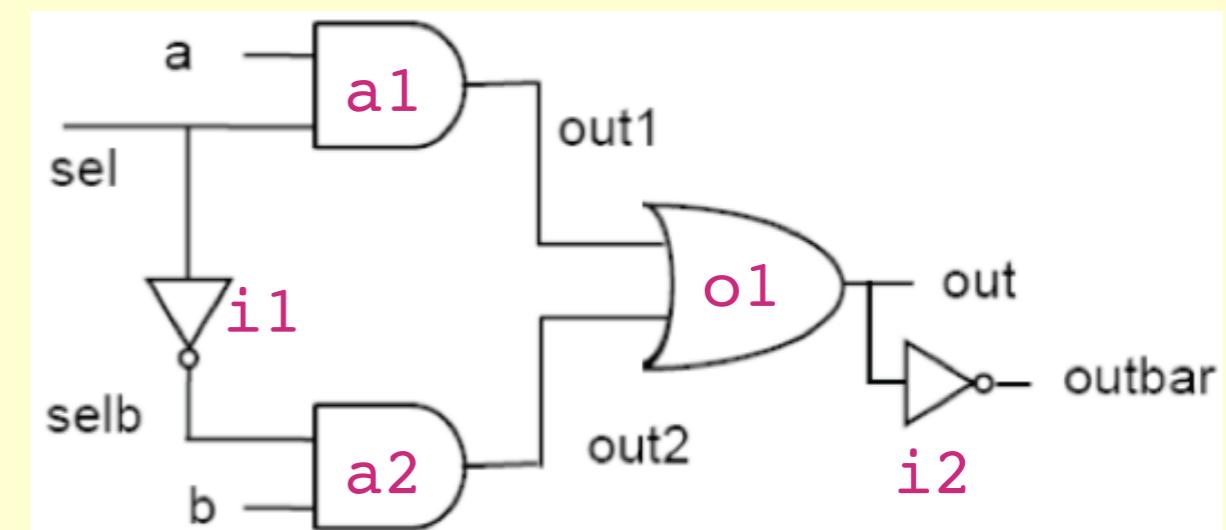  not i1 (selb, sel);
  and a1 (out1, a, sel);
  and a2 (out2, b, selb);
  or o1 (out, out1, out2);
  not i2 (outbar, out);
endmodule
```



- In practice, "gate-level description" depends on what primitives are provided by your target chip.

Always blocks

- Verilog provides **always** blocks for defining **sequential** logic.

Variables (not registers)

```
module mux2to1 (out, outbar,
                 a, b, sel);
    output out, outbar;
    input a, b, sel;
    reg out, outbar;

    always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;

        outbar = ~out;
    end
endmodule
```

Sensitivity list

Can also contain
case, for, while

Executed in sequence
(order matters!)

Always blocks

- Can mix procedural and continuous assignments.

```
module mux2to1 (out, outbar,
                 a, b, sel);
  output out, outbar;
  input a, b, sel;
  reg out, outbar;

  always @ (a or b or sel)
  begin
    if (sel) out = a;
    else out = b;

    outbar = ~out;
  end
endmodule
```

```
module mux2to1 (out, outbar,
                 a, b, sel);
  output out, outbar;
  input a, b, sel;
  reg out;

  always @ (a or b or sel)
  begin
    if (sel) out = a;
    else out = b;
  end

  assign outbar = ~out;
endmodule
```

Numerical constants

- Format is $<\text{size}>^{\prime} <\text{signedness}><\text{base}><\text{number}>$
- $<\text{size}>$ defaults to **32**.
- $<\text{base}>$ is either **b** (binary=2), **o** (octal=8), **d** (decimal=10), or **h** (hexadecimal=16). Decimal is the default.
- $<\text{signedness}>$ is either blank (unsigned, default) or **s** (signed).

Numerical constants

- Format is $<\text{size}>^{\prime} <\text{signedness}><\text{base}><\text{number}>$
- $<\text{size}>$ defaults to **32**.
- $<\text{base}>$ is either **b** (binary=2), **o** (octal=8), **d** (decimal=10), or **h** (hexadecimal=16). Decimal is the default.
- $<\text{signedness}>$ is either blank (unsigned, default) or **s** (signed).
- Examples: **2'b10**,

Numerical constants

- Format is $\langle\text{size}\rangle' \langle\text{signedness}\rangle \langle\text{base}\rangle \langle\text{number}\rangle$
- $\langle\text{size}\rangle$ defaults to **32**.
- $\langle\text{base}\rangle$ is either **b** (binary=2), **o** (octal=8), **d** (decimal=10), or **h** (hexadecimal=16). Decimal is the default.
- $\langle\text{signedness}\rangle$ is either blank (unsigned, default) or **s** (signed).
- Examples: **2'b10**, **'b10**,

Numerical constants

- Format is $\langle\text{size}\rangle' \langle\text{signedness}\rangle \langle\text{base}\rangle \langle\text{number}\rangle$
- $\langle\text{size}\rangle$ defaults to **32**.
- $\langle\text{base}\rangle$ is either **b** (binary=2), **o** (octal=8), **d** (decimal=10), or **h** (hexadecimal=16). Decimal is the default.
- $\langle\text{signedness}\rangle$ is either blank (unsigned, default) or **s** (signed).
- Examples: **2'b10**, **'b10**, **31**,

Numerical constants

- Format is $<\text{size}>^{\prime} <\text{signedness}><\text{base}><\text{number}>$
- $<\text{size}>$ defaults to **32**.
- $<\text{base}>$ is either **b** (binary=2), **o** (octal=8), **d** (decimal=10), or **h** (hexadecimal=16). Decimal is the default.
- $<\text{signedness}>$ is either blank (unsigned, default) or **s** (signed).
- Examples: **2'b10**, **'b10**, **31**, **8'hAf**,

Numerical constants


- Format is $<\text{size}>^{\prime} <\text{signedness}><\text{base}><\text{number}>$
- $<\text{size}>$ defaults to **32**.
- $<\text{base}>$ is either **b** (binary=2), **o** (octal=8), **d** (decimal=10), or **h** (hexadecimal=16). Decimal is the default.
- $<\text{signedness}>$ is either blank (unsigned, default) or **s** (signed).
- Examples: **2'b10**, **'b10**, **31**, **8'hAf**, **2'sb10**

Buses

- Concatenate wires into a **bus** using `{ . . . }` syntax. E.g.:

```
input [15:0] x;  
output [15:0] y;  
assign y = { x[7:0], x[15:8] };
```


- An 8-bit multiplexer:

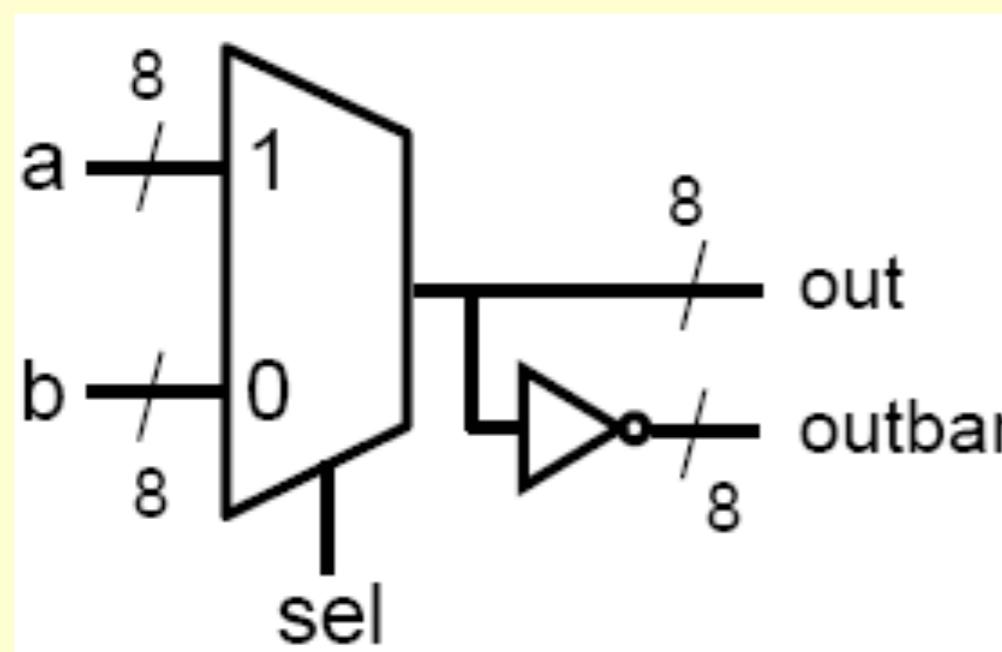

```
module mux2to1 (out, outbar,  
                  a, b, sel);  
    output[7:0] out, outbar;  
    input[7:0] a, b;  
    input sel;  
    reg[7:0] out;  
  
    always @ (a or b or sel)  
    begin  
        if (sel) out = a;  
        else out = b;  
    end  
    assign outbar = ~out;  
endmodule
```

Case statements
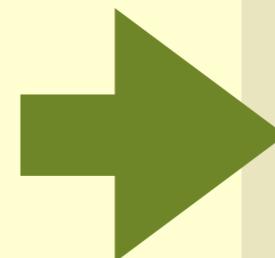
```
always @ (a or b or sel)
begin
    if (sel) out = a;
    else out = b;
end
```




could write
always @ *

```
always @ (a or b or sel)
begin
    case (sel)
        1'b0: out = b;
        1'b1: out = a;
    endcase
end
```

Putting it all together

7-seg decoder

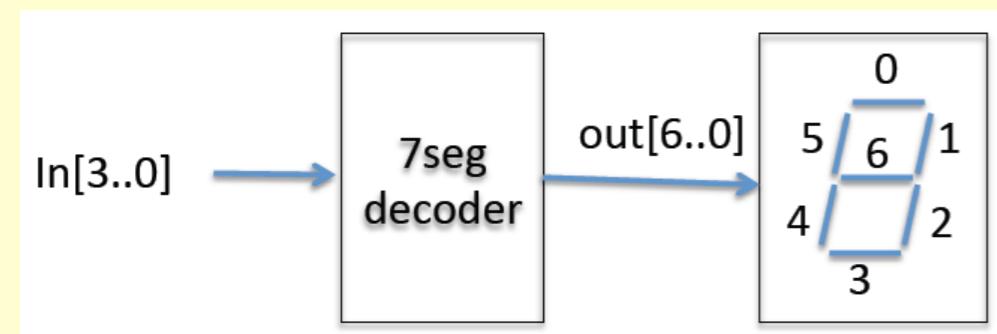


| $\text{in}[3..0]$ | $\text{out}[6:0]$ | Digit | $\text{in}[3..0]$ | $\text{out}[6:0]$ | Digit |
|-------------------|-------------------|-------|-------------------|-------------------|-------|
| 0000 | 1000000 | 0 | 1000 | 0000000 | 0 |
| 0001 | 1111001 | / | 1001 | 0010000 | 9 |
| 0010 | 0100100 | 2 | 1010 | 0001000 | A |
| 0011 | 0110000 | 3 | 1011 | 0000011 | b |
| 0100 | 0011001 | 4 | 1100 | 1000110 | C |
| 0101 | 0010010 | 5 | 1101 | 0100001 | d |
| 0110 | 0000010 | 6 | 1110 | 0000110 | E |
| 0111 | 1111000 | 7 | 1111 | 0001110 | F |

| $\text{In}3 : \text{in}2$ | | | | |
|---------------------------|----|----|----|----|
| $\text{out}6$ | 00 | 01 | 11 | 10 |
| 00 | 1 | 0 | 1 | 0 |
| 01 | 1 | 0 | 0 | 0 |
| 11 | 0 | 1 | 0 | 0 |
| 10 | 0 | 0 | 0 | 0 |

$$\text{out}6 = (\overline{\text{in}3} \wedge \overline{\text{in}2} \wedge \overline{\text{in}1}) \vee (\text{in}3 \wedge \text{in}2 \wedge \overline{\text{in}1} \wedge \overline{\text{in}0}) \vee (\overline{\text{in}3} \wedge \text{in}2 \wedge \text{in}1 \wedge \text{in}0)$$



First attempt

- Draw a schematic:

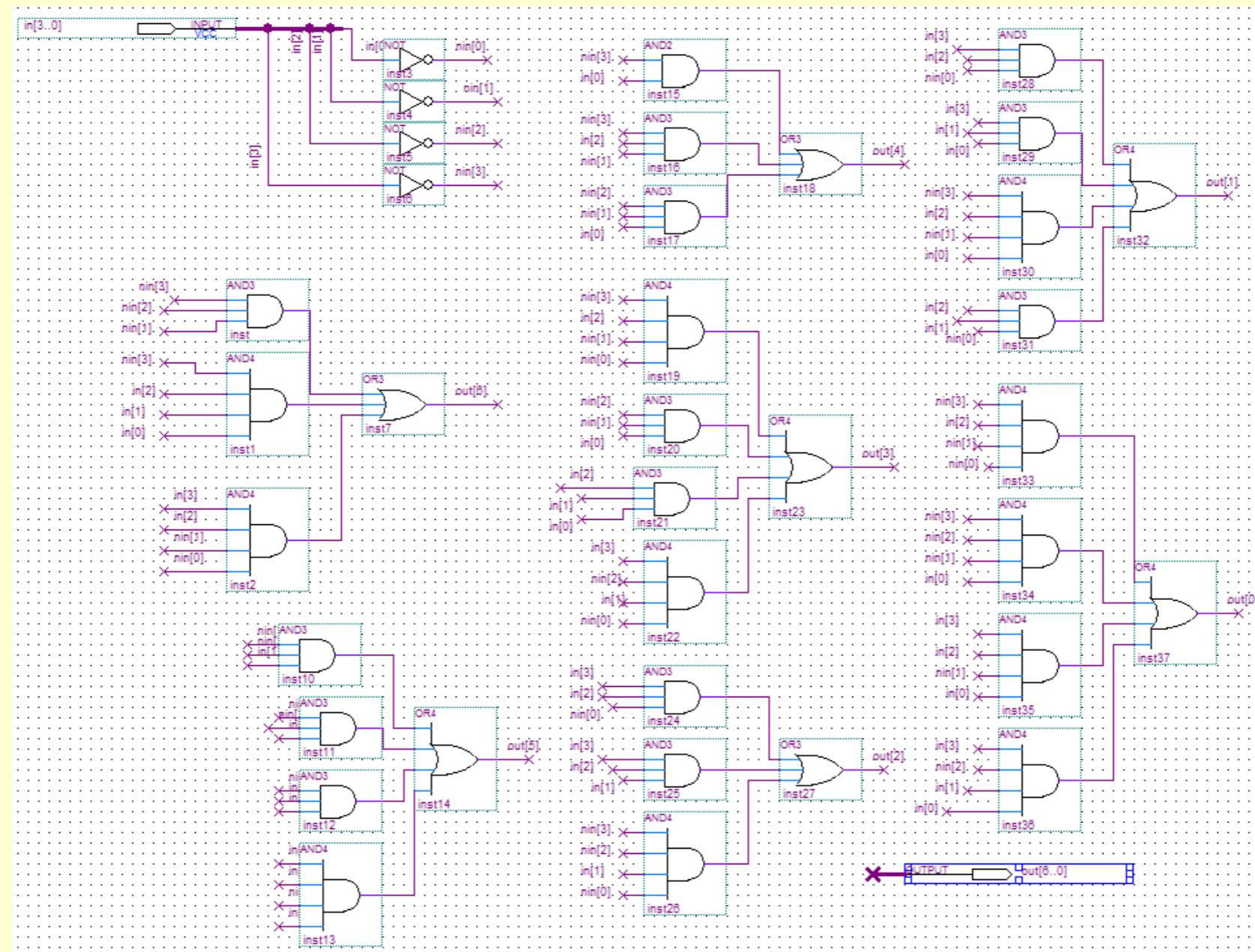

Second attempt

- Gate-level description:

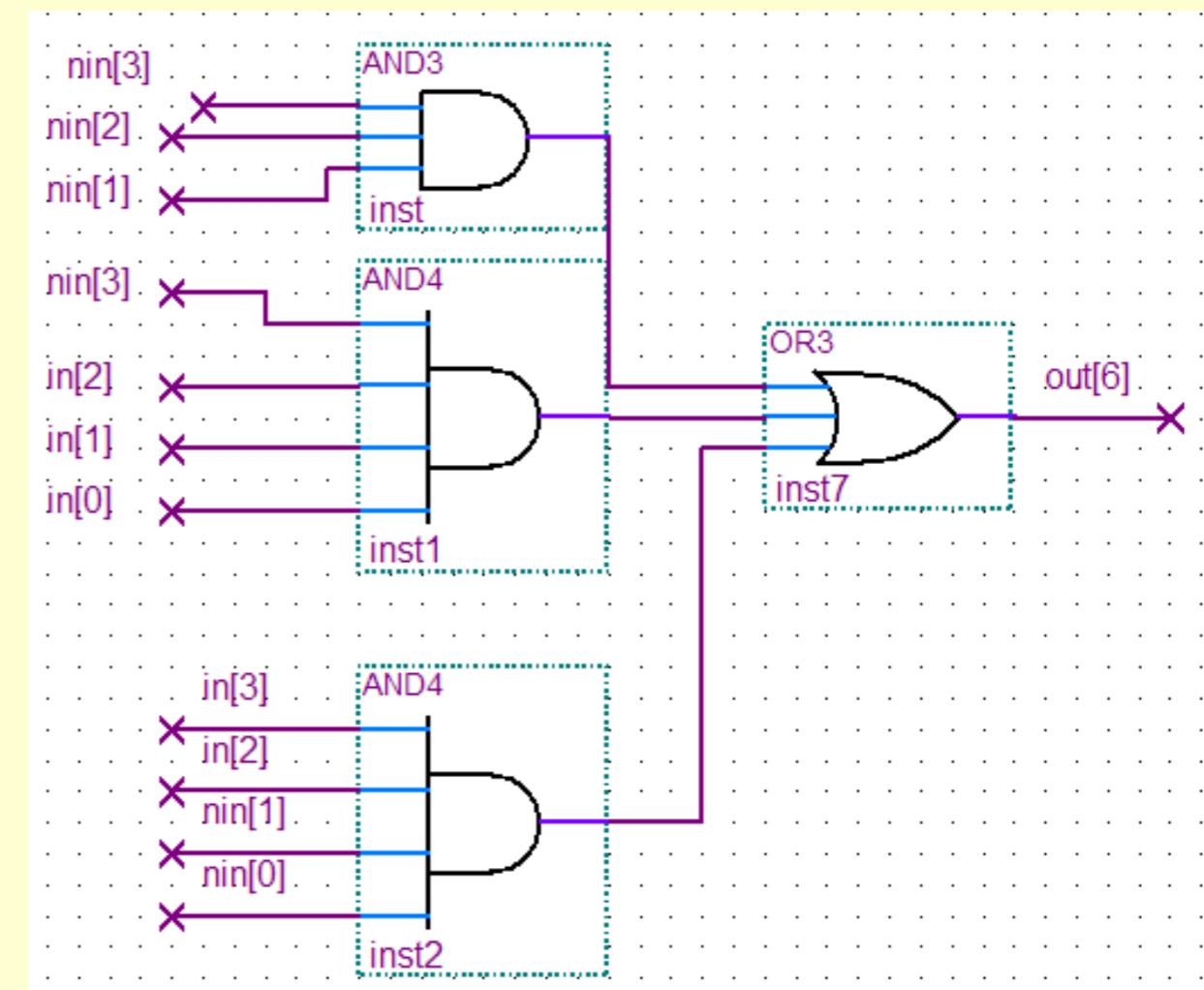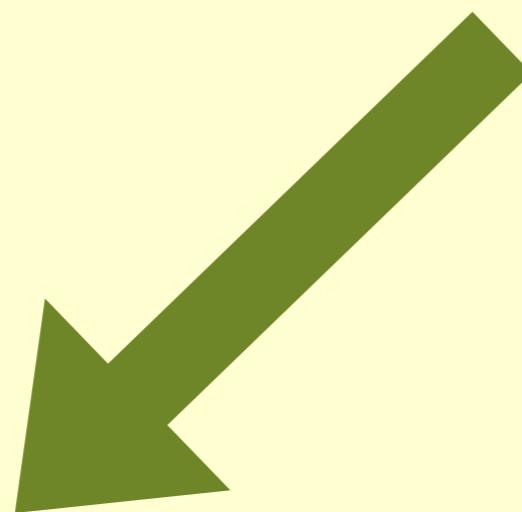

```
and AND1 (A, nin[3], nin[2], nin[1]);  
and AND2 (B, nin[3], in[2], in[1], in[0]);  
and AND3 (C, in[3], in[2], nin[1], nin[0]);  
or OR1 (out[6], A, B, C);
```

Third attempt

- Use continuous assignment:

```
and AND1 (A, nin[3], nin[2], nin[1]);  
and AND2 (B, nin[3], in[2], in[1], in[0]);  
and AND3 (C, in[3], in[2], nin[1], nin[0]);  
or OR1 (out[6], A, B, C);
```



```
assign out[6] = ~in[3]&~in[2]&~in[1] |  
            in[3]&in[2]&~in[1]&~in[0] |  
            ~in[3]&in[2]&in[1]&in[0];
```

```
//-----
// Module name: hex_to_7seg
// Function: convert 4-bit hex value to drive 7 segment display
//           output is low active
// Creator: Peter Cheung
// Version: 1.0
// Date:    22 Oct 2011
//-----

module hex_to_7seg  (out,in);

    output [6:0]    out;      // low-active output to drive 7 segment display
    input  [3:0]    in;       // 4-bit binary input of a hexadematical number

    assign out[6] = ~in[3]&~in[2]&~in[1] | in[3]&in[2]&~in[1]&~in[0] |
                  ~in[3]&in[2]&in[1]&in[0];
    assign out[5] = ~in[3]&~in[2]&in[0] | ~in[3]&~in[2]&in[1] |
                  ~in[3]&in[1]&in[0] | in[3]&in[2]&~in[1]&in[0];
    assign out[4] = ~in[3]&in[0] | ~in[3]&in[2]&~in[1] | in[3]&~in[2]&~in[1]&in[0];
    assign out[3] = ~in[3]&in[2]&~in[1]&~in[0] | ~in[3]&~in[2]&~in[1]&in[0] |
                  in[2]&in[1]&in[0] | ~in[2]&in[1]&~in[0];
    assign out[2] = ~in[3]&~in[2]&in[1]&~in[0] | in[3]&in[2]&~in[0] |
                  in[3]&in[2]&in[1];
    assign out[1] = in[3]&in[2]&~in[0] | ~in[3]&in[2]&~in[1]&in[0] |
                  in[3]&in[1]&in[0] | in[2]&in[1]&~in[0];
    assign out[0] = ~in[3]&~in[2]&~in[1]&in[0] | ~in[3]&in[2]&~in[1]&~in[0] |
                  in[3]&in[2]&~in[1]&in[0] | in[3]&~in[2]&in[1]&in[0];

endmodule
```

Fourth attempt

```
module hex_to_7seg (out,in);  
  
    output [6:0] out; // low-active output to  
    input  [3:0] in; // 4-bit binary input o  
  
    reg      [6:0] out; // make out a variable  
  
    always @ (in)  
        case (in)  
            4'h0: out = 7'b1000000;  
            4'h1: out = 7'b1111001; // -- 0 ---  
            4'h2: out = 7'b0100100; // | |  
            4'h3: out = 7'b0110000; // 5 1  
            4'h4: out = 7'b0011001; // | |  
            4'h5: out = 7'b0010010; // -- 6 ---  
            4'h6: out = 7'b0000010; // | |  
            4'h7: out = 7'b1111000; // 4 2  
            4'h8: out = 7'b0000000; // | |  
            4'h9: out = 7'b0011000; // -- 3 ---  
            4'ha: out = 7'b0001000;  
            4'hb: out = 7'b0000011;  
            4'hc: out = 7'b1000110;  
            4'hd: out = 7'b0100001;  
            4'he: out = 7'b0000110;  
            4'hf: out = 7'b0001110;  
        endcase  
    endmodule
```

| in[3..0] | out[6:0] | Digit |
|----------|----------|-------|
| 0000 | 1000000 | 0 |
| 0001 | 1111001 | 1 |
| 0010 | 0100100 | 2 |
| 0011 | 0110000 | 3 |
| 0100 | 0011001 | 4 |
| 0101 | 0010010 | 5 |
| 0110 | 0000010 | 6 |
| 0111 | 1111000 | 7 |
| 1000 | 0000000 | 8 |
| 1001 | 0010000 | 9 |
| 1010 | 0001000 | A |
| 1011 | 0000011 | b |
| 1100 | 1000110 | C |
| 1101 | 0100001 | d |
| 1110 | 0000110 | E |
| 1111 | 0001110 | F |

From Verilog to Hardware

