

Mastering Digital Design

with Verilog on FPGAs

John Wickerson

Lecture 4

This lecture

- The design of the spi2dac module
- How the ADC works
- Wrapping up

This lecture



- **The design of the spi2dac module**
- How the ADC works
- Wrapping up




spi2dac

```

parameter TC = 5'd24;
reg [4:0] ctr;
always @ (posedge clk_50MHz)
  if (ctr==0) begin
    ctr <= TC;
    clk_1MHz <= ~clk_1MHz;
  end else ctr <= ctr - 1'b1;

```

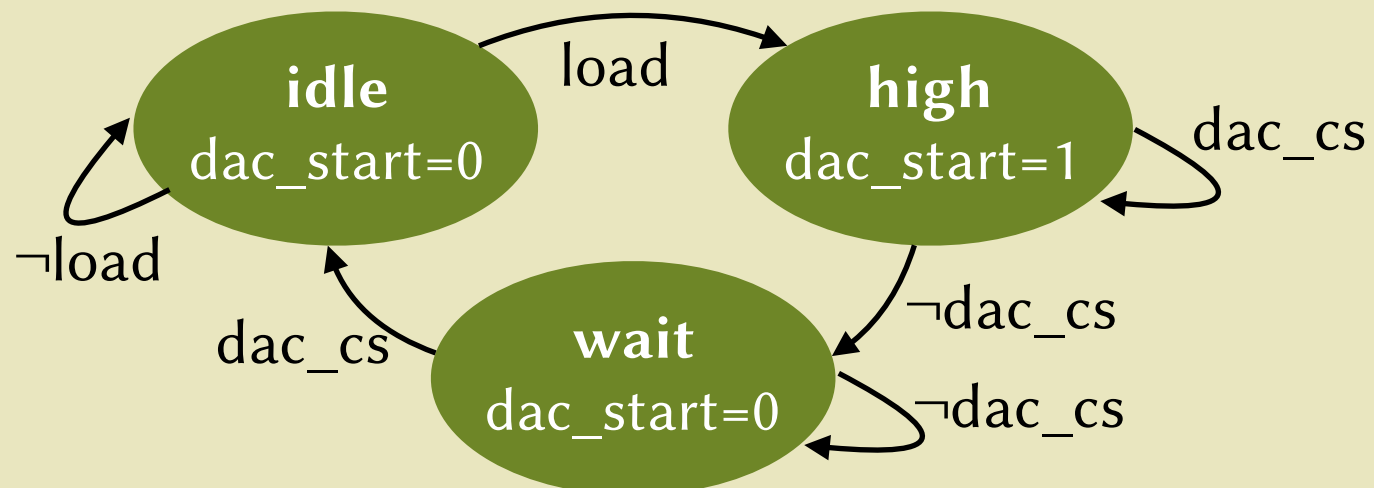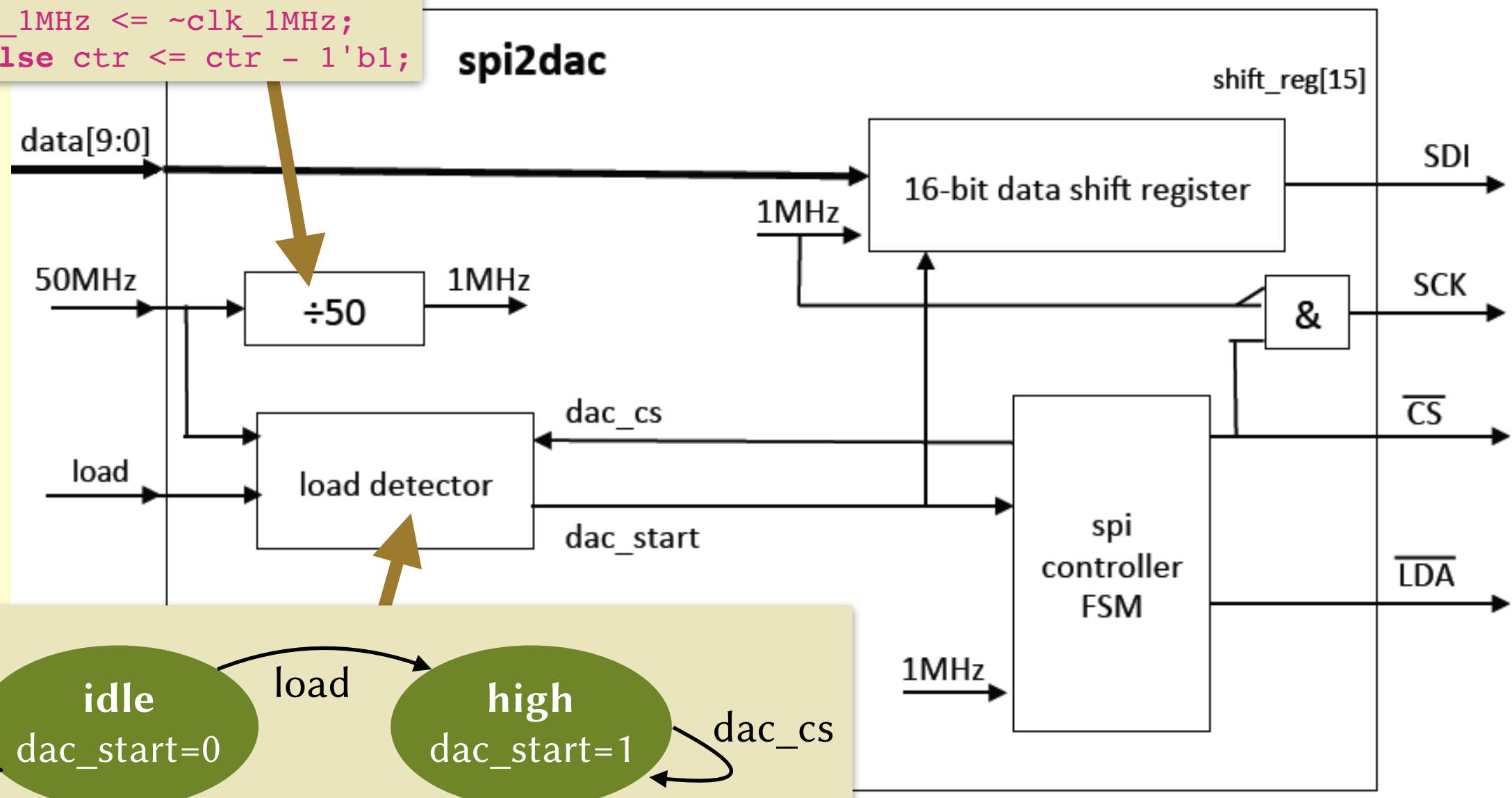

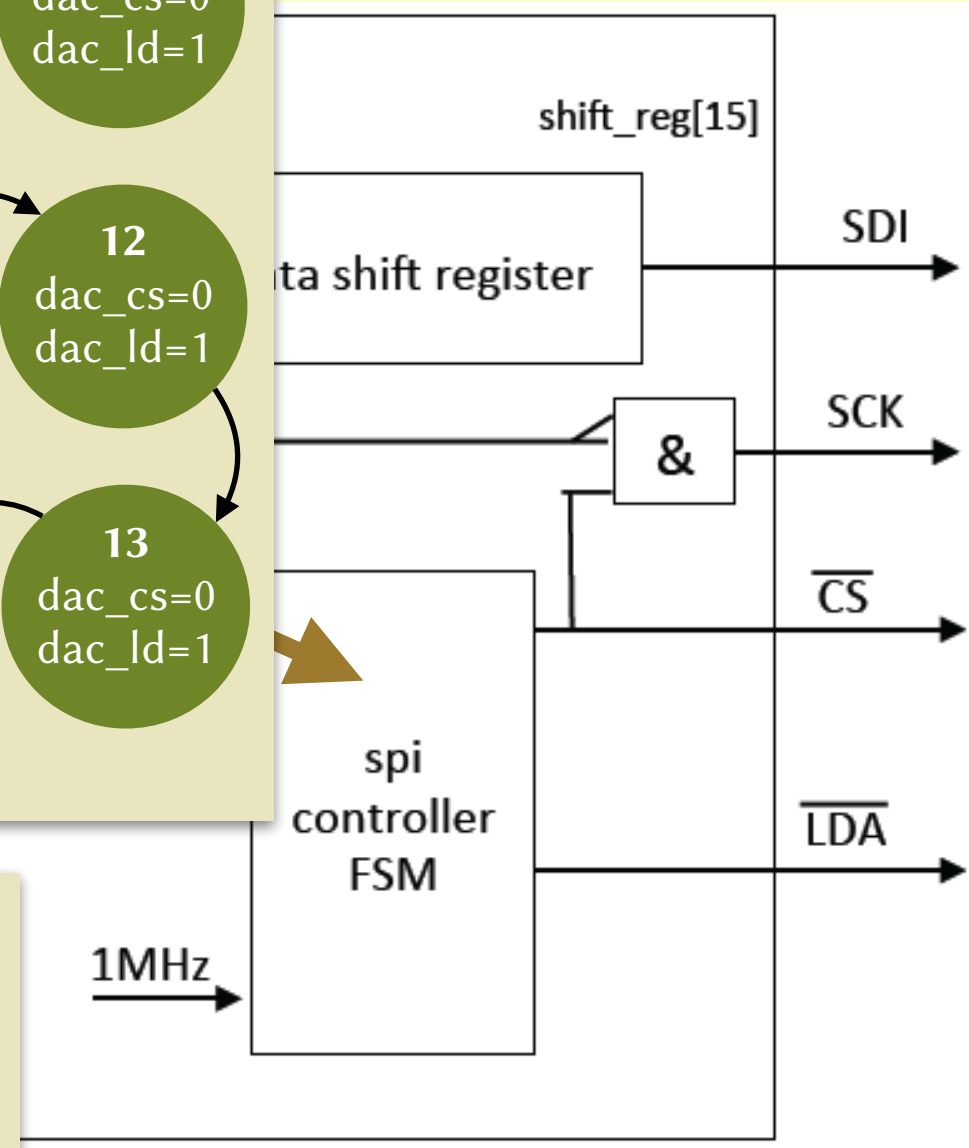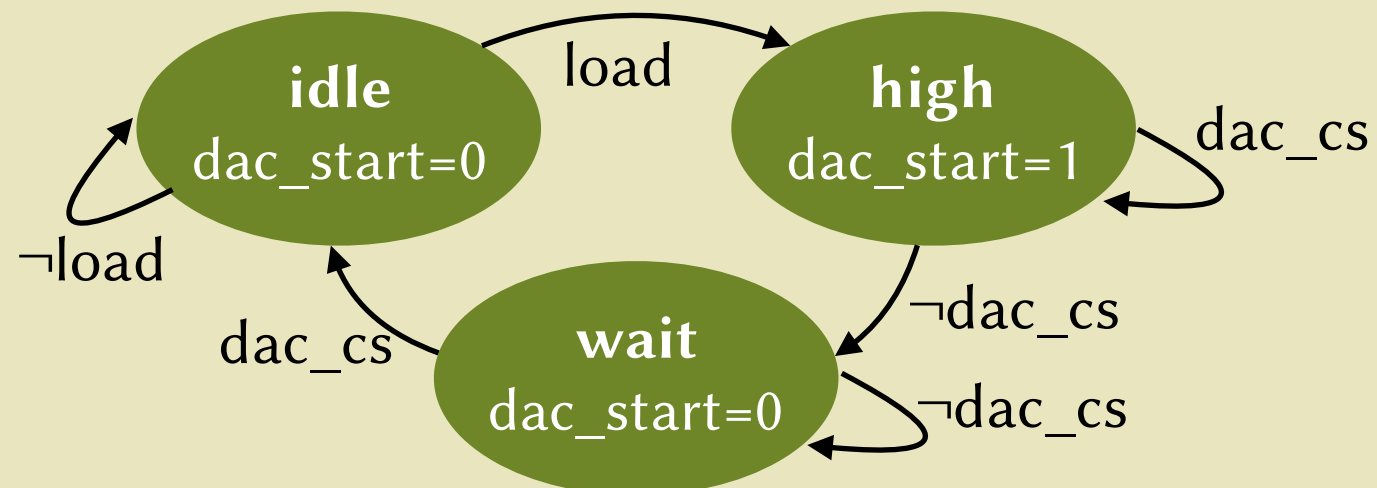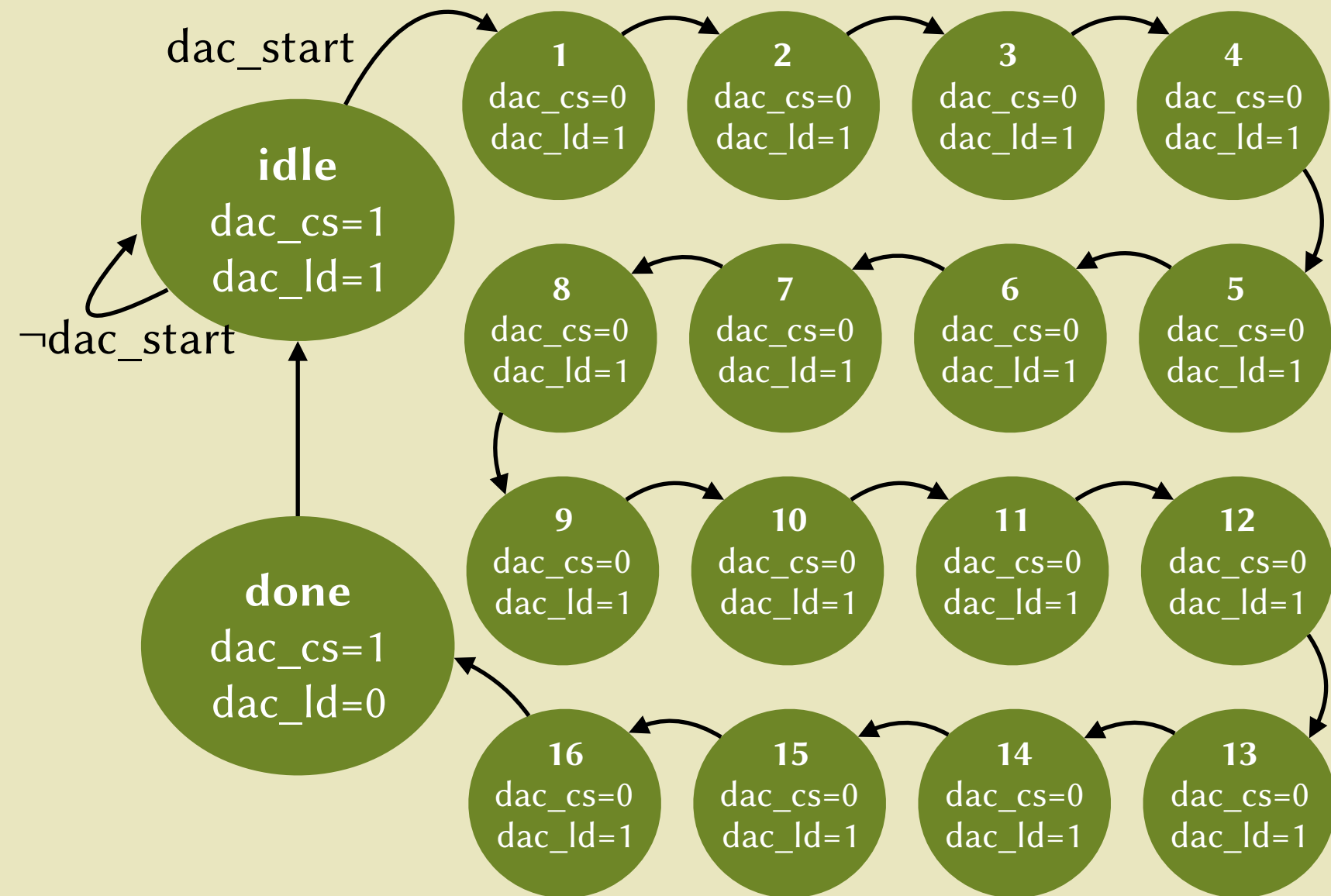

```

parameter
reg [4:0]
always
if (c
ctr
clk
end e



```

```

reg [4:0] state;
always @ (posedge clk_1MHz)
  case (state)
    5'd0:    if (dac_start == 1'b1)
              state <= state + 1'b1;
    5'd17:   state <= 5'd0;
    default: state <= state + 1'b1;
  endcase
always @ * begin
  case (state)
    5'd0:    {dac_cs, dac_ld} = 2'b11;
    5'd17:   {dac_cs, dac_ld} = 2'b10;
    default: {dac_cs, dac_ld} = 2'b01;
  endcase
end

```

2dac

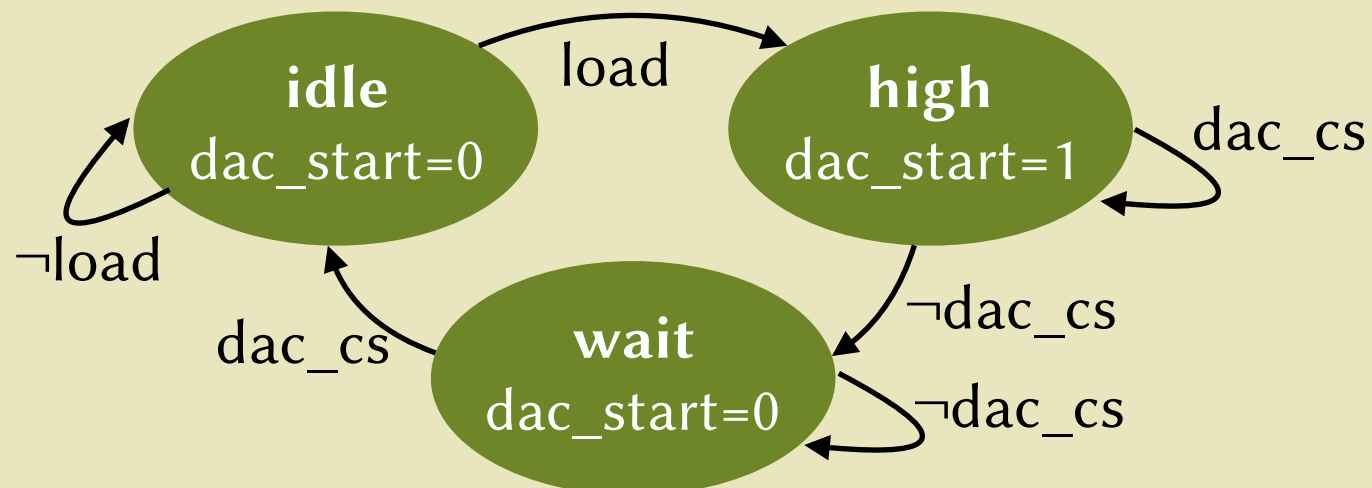
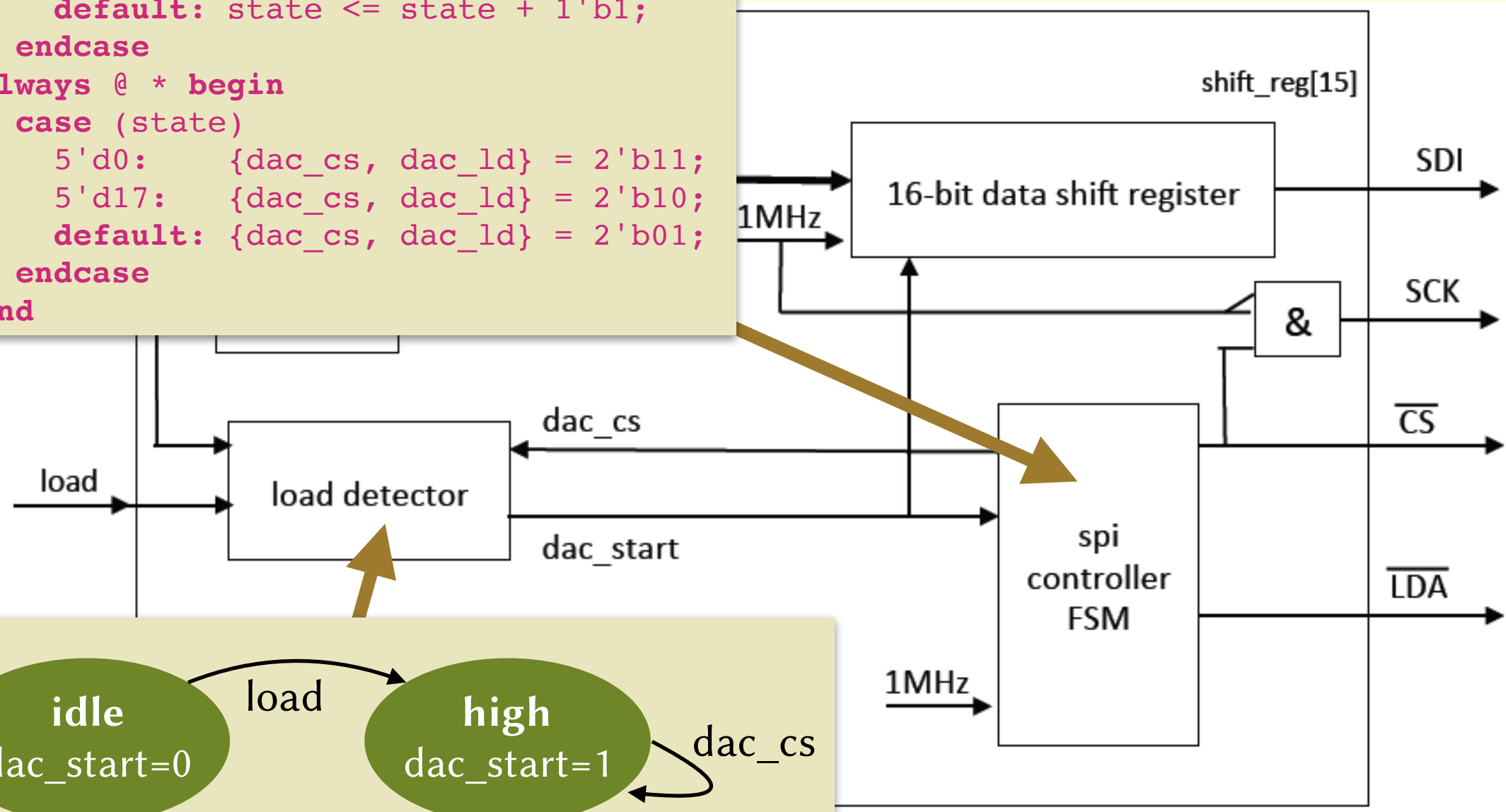


2dac

```

reg [4:0] state;
always @ (posedge clk_1MHz)
  case (state)
    5'd0:    if (dac_start == 1'b1)
              state <= state + 1'b1;
    5'd17:   state <= 5'd0;
    default: state <= state + 1'b1;
  endcase
always @ * begin
  case (state)
    5'd0:    {dac_cs, dac_ld} = 2'b11;
    5'd17:   {dac_cs, dac_ld} = 2'b10;
    default: {dac_cs, dac_ld} = 2'b01;
  endcase
end

```

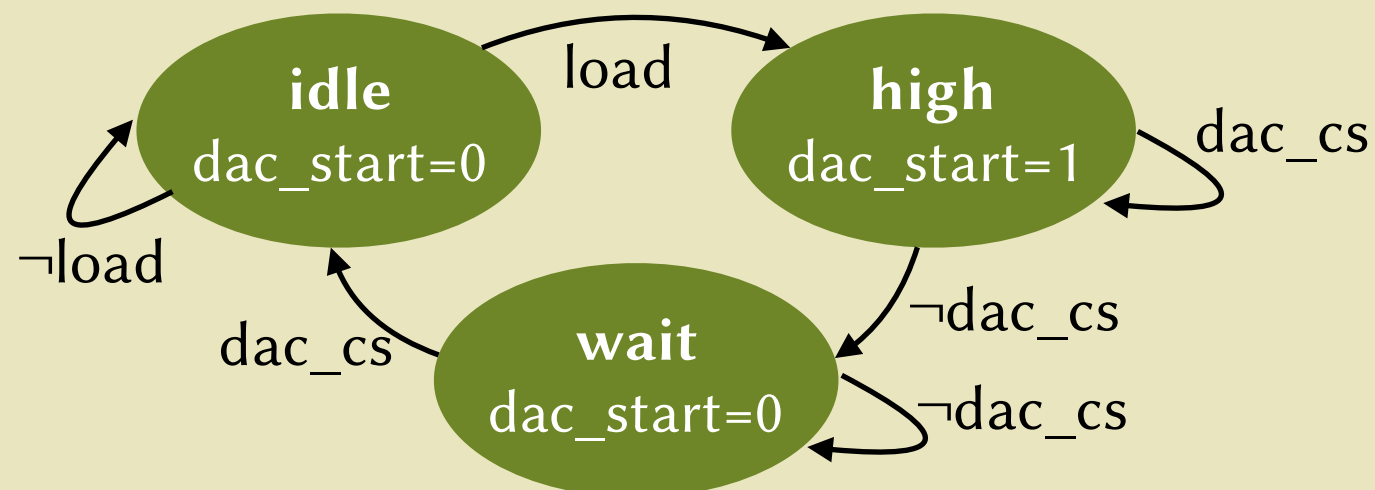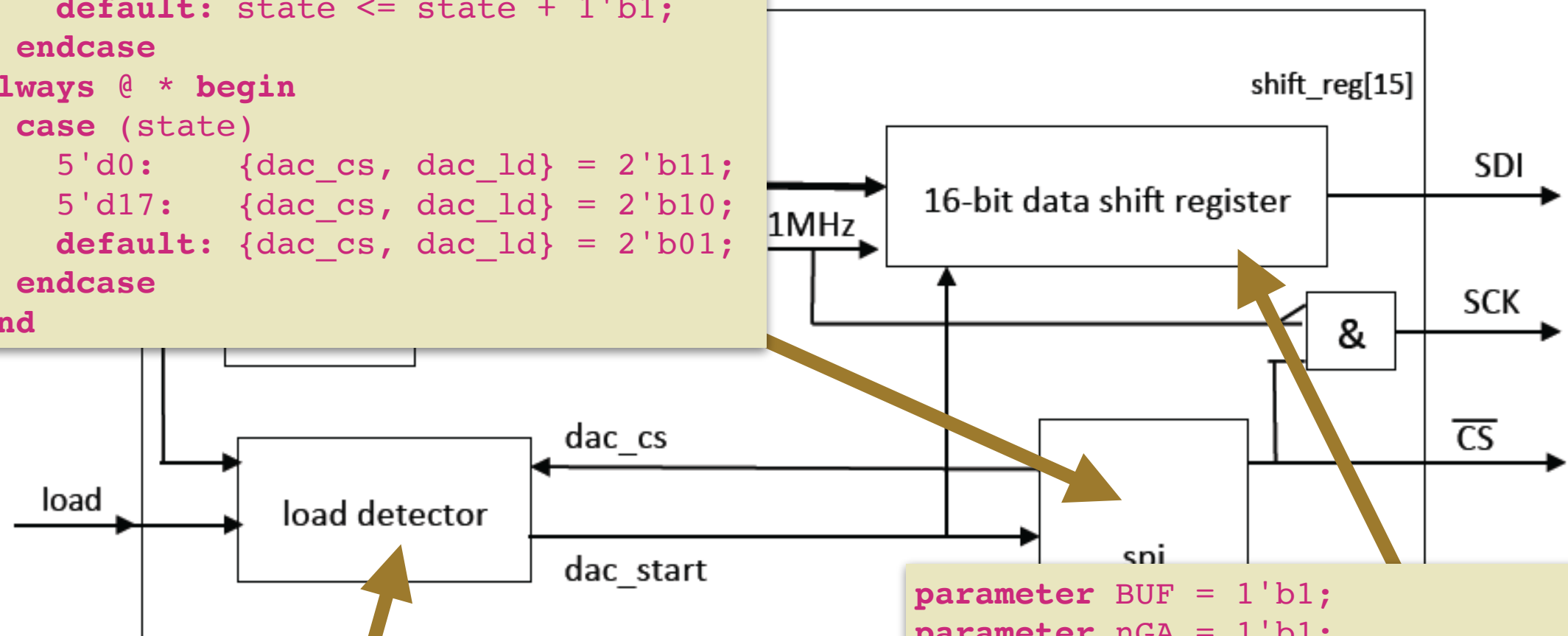

```

parameter BUF = 1'b1;
parameter nGA = 1'b1;
parameter nSHDN = 1'b1;
wire[3:0] cmd = {1'b0, BUF, nGA, nSHDN};
reg [15:0] sreg;
always @ (posedge clk_1MHz)
  if ({dac_start, dac_cs} == 2'b11)
    sreg <= {cmd, data_in, 2'b00};
  else
    sreg <= {sreg[14:0], 1'b0};
assign dac_sck = !clk_1MHz & !dac_cs;
assign dac_sdi = sreg[15];

```

This lecture

- The design of the spi2dac module
- How the ADC works
- Wrapping up


This lecture

- The design of the spi2dac module
- **How the ADC works**
- Wrapping up


ADC using SAR




ADC using SAR

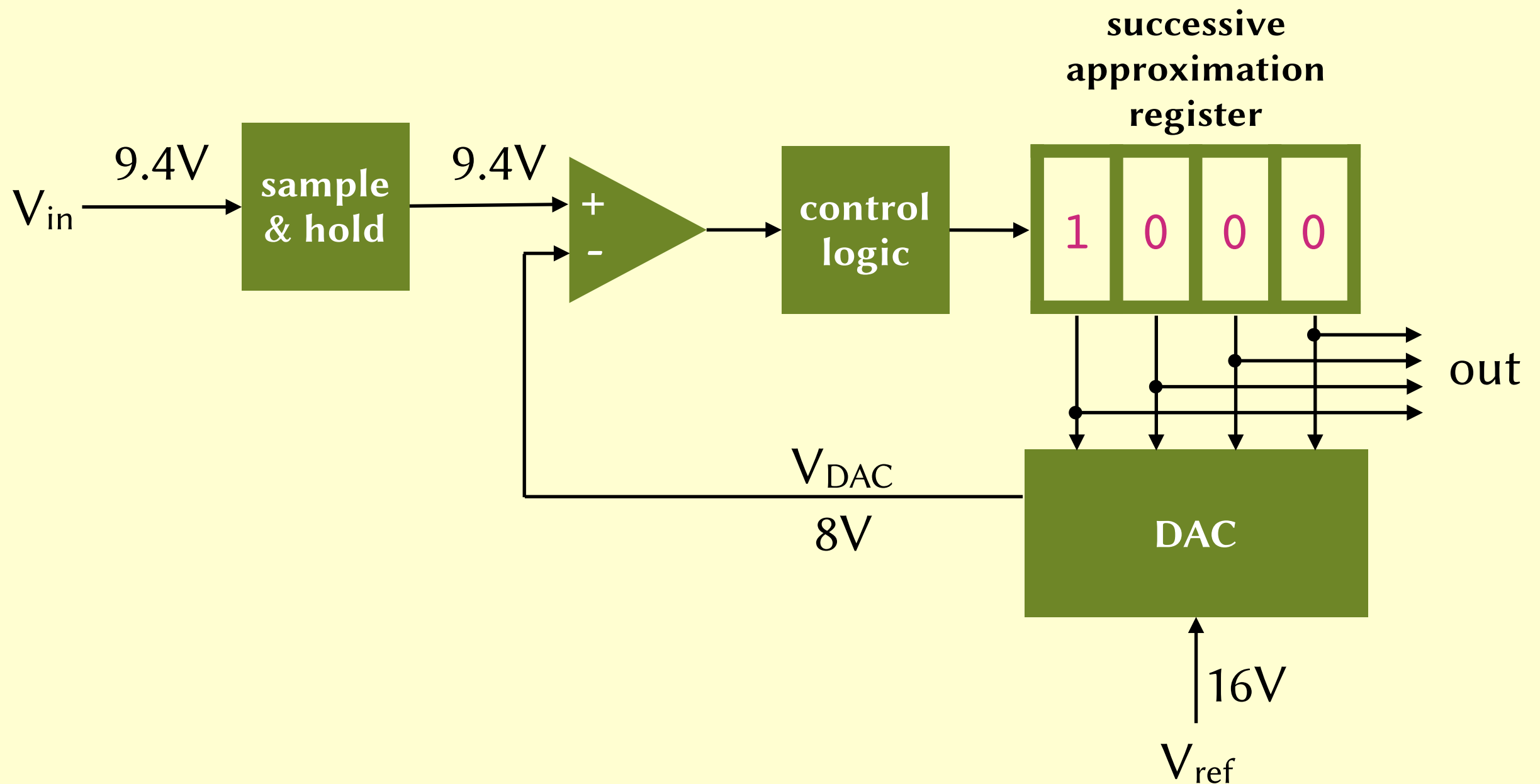


ADC using SAR

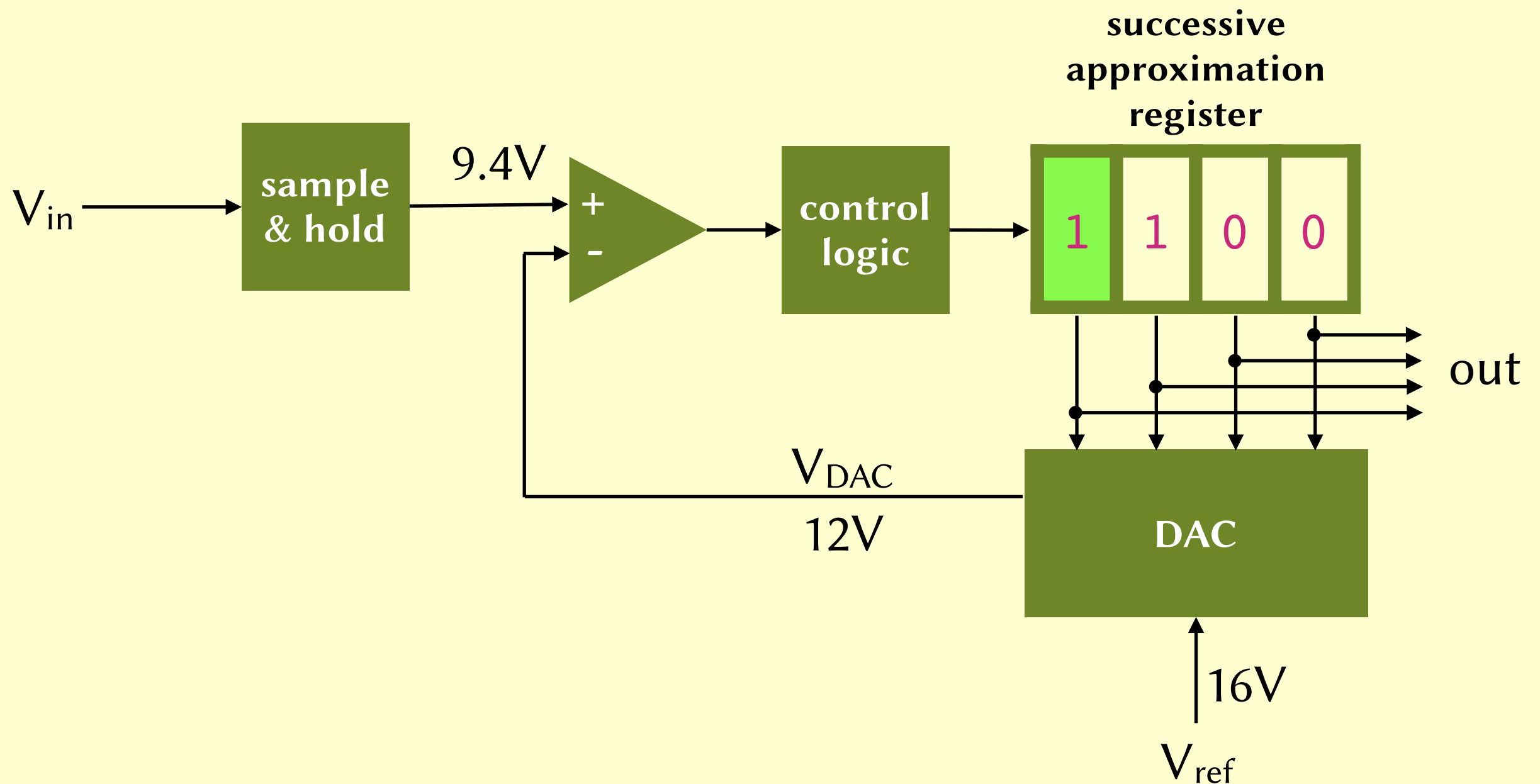


ADC using SAR

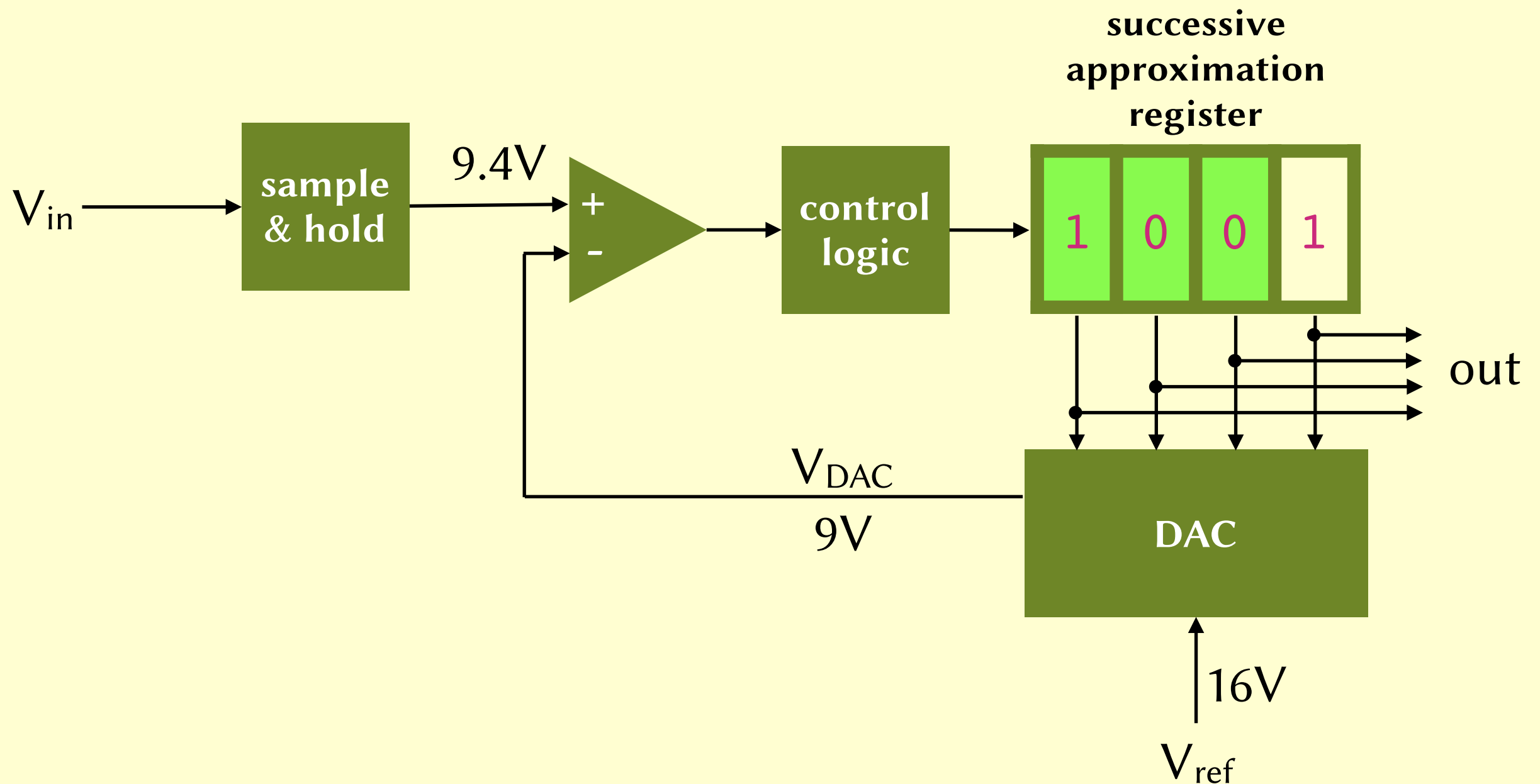


ADC using SAR

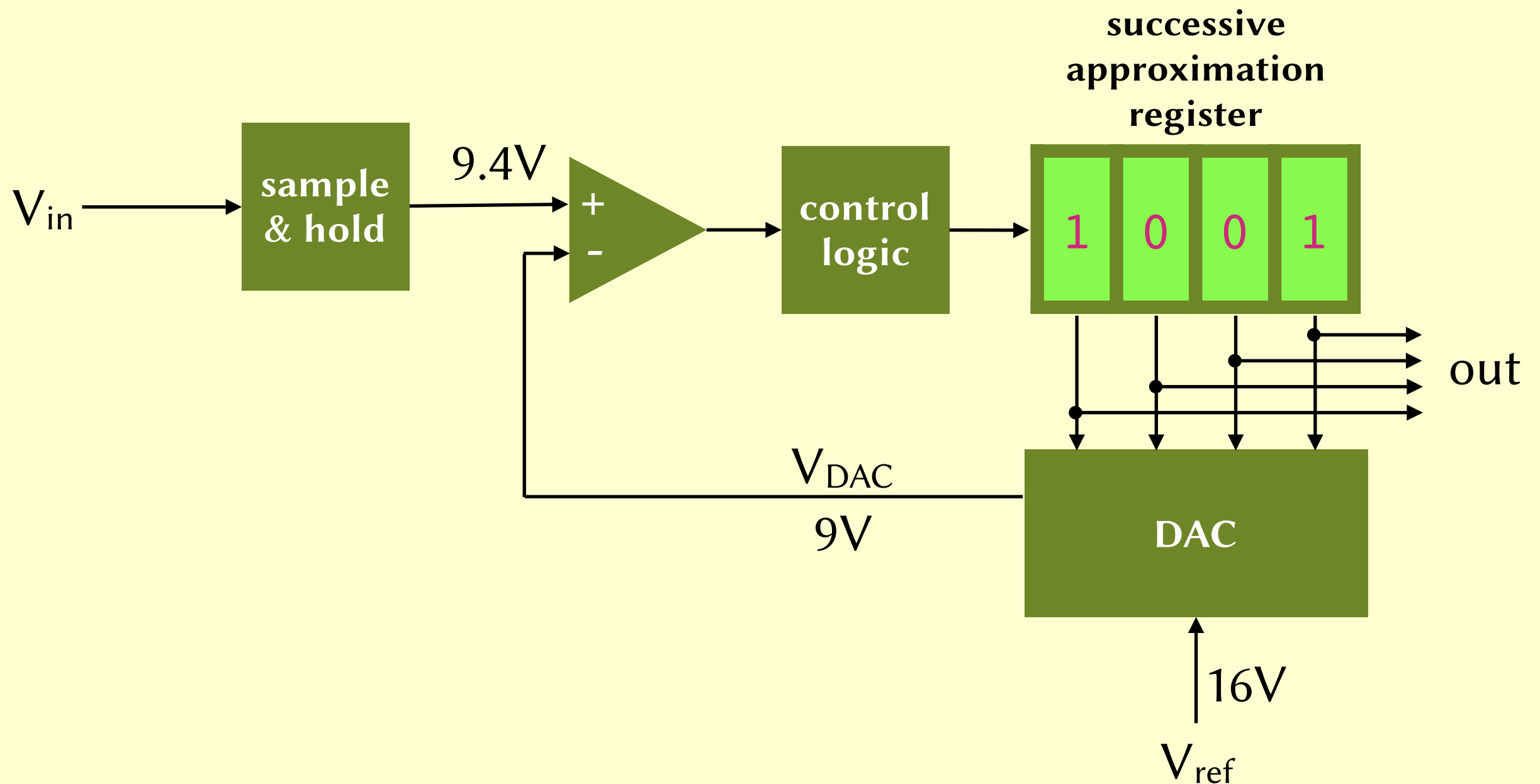


ADC using SAR

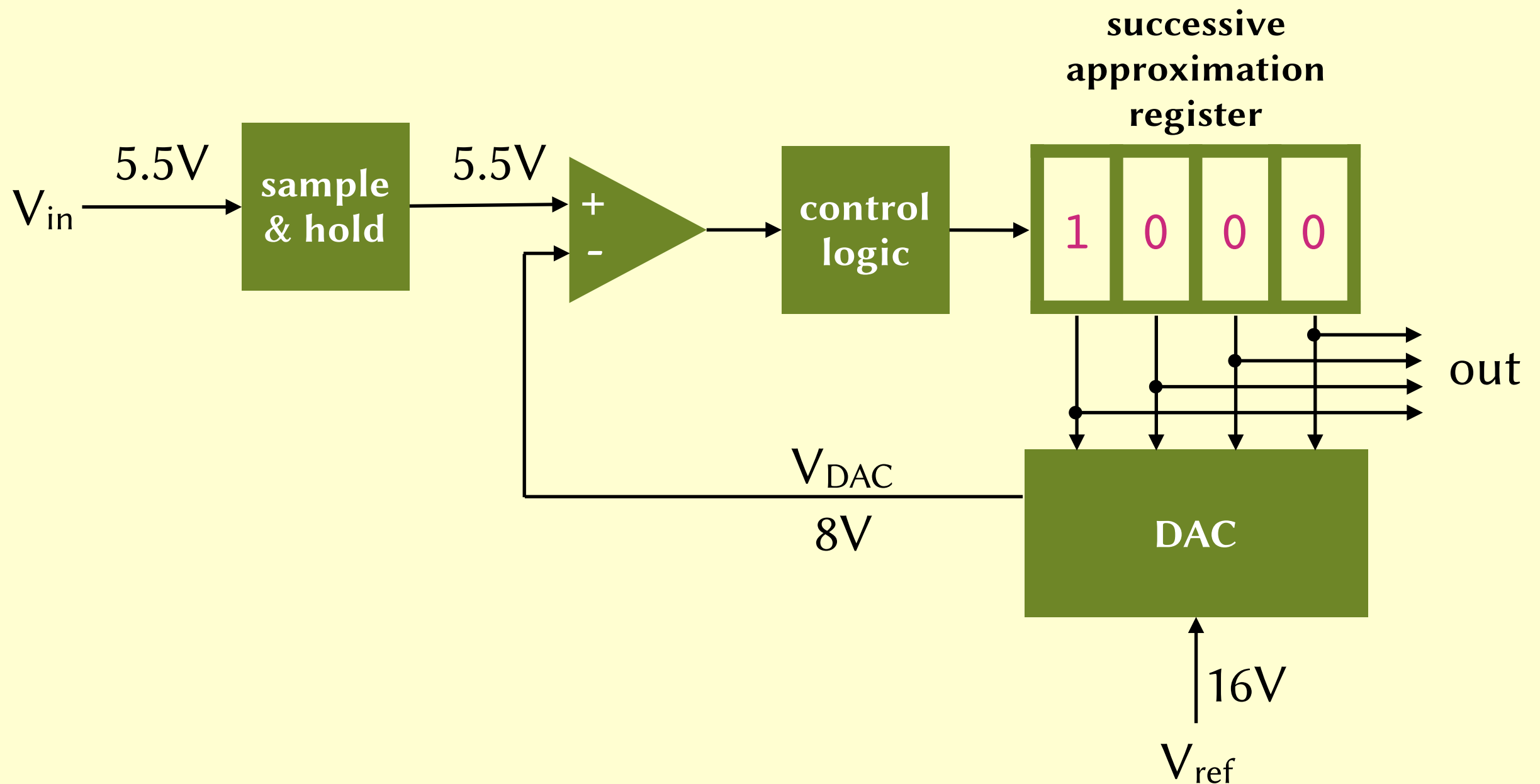


ADC using SAR

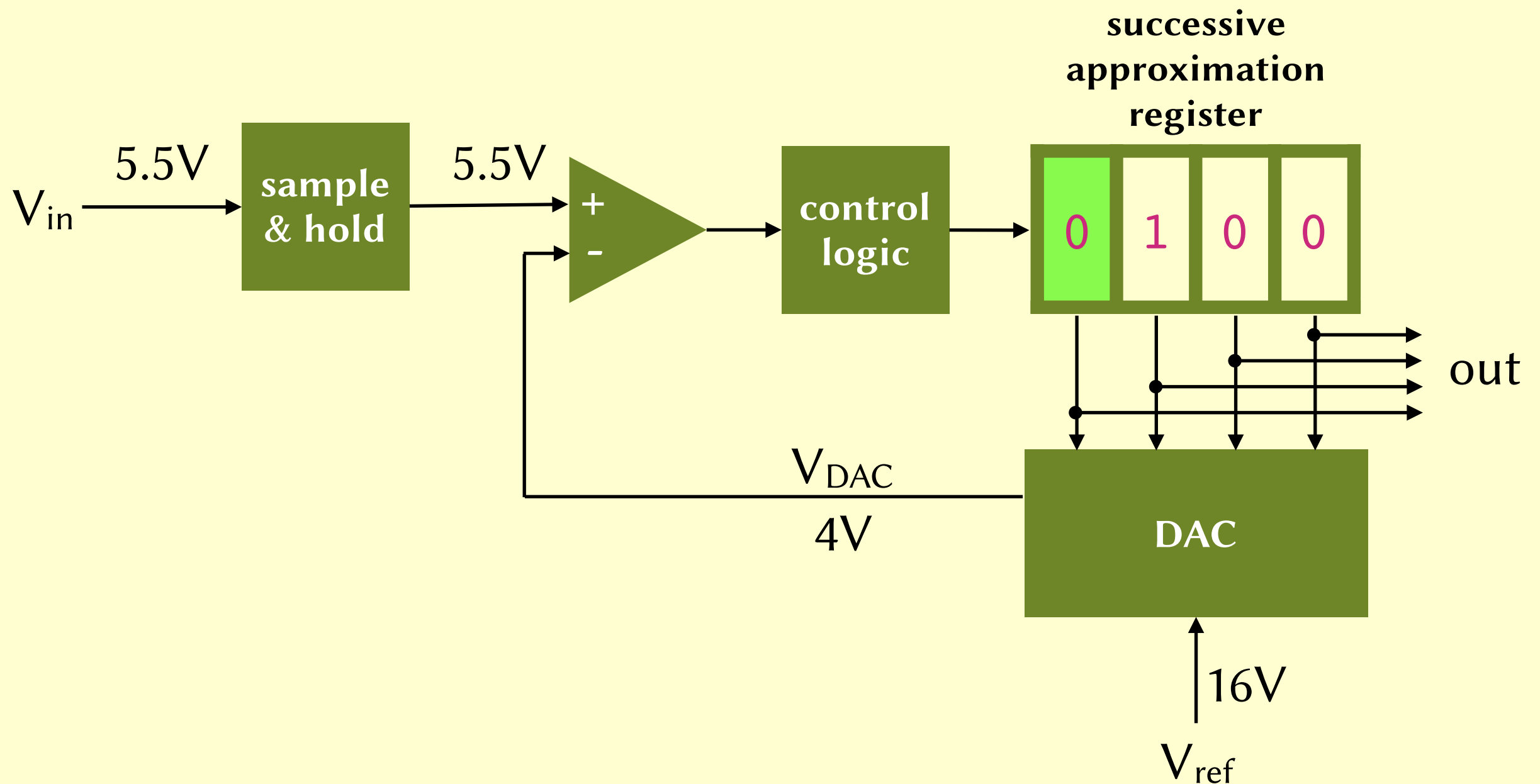


ADC using SAR

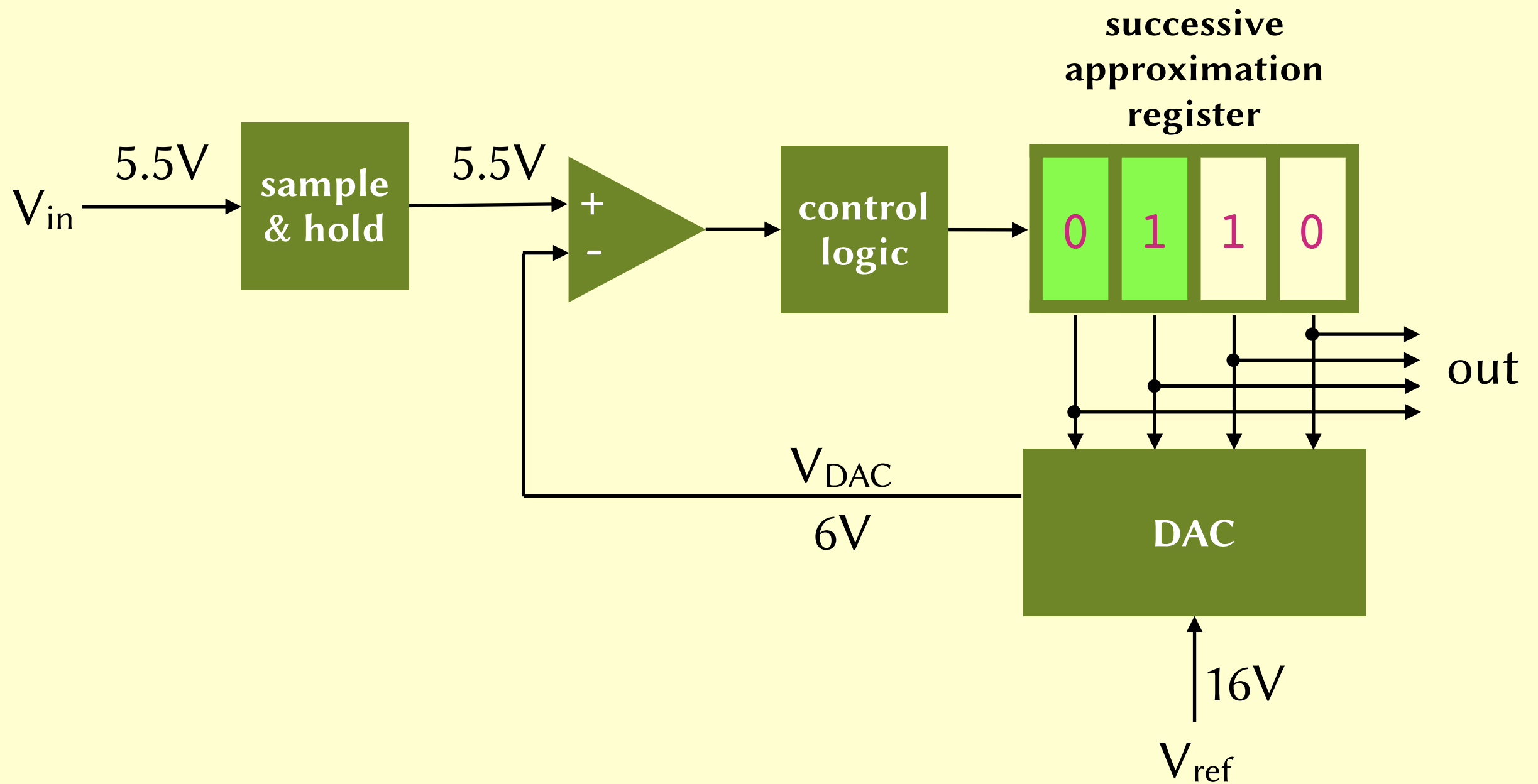

ADC using SAR

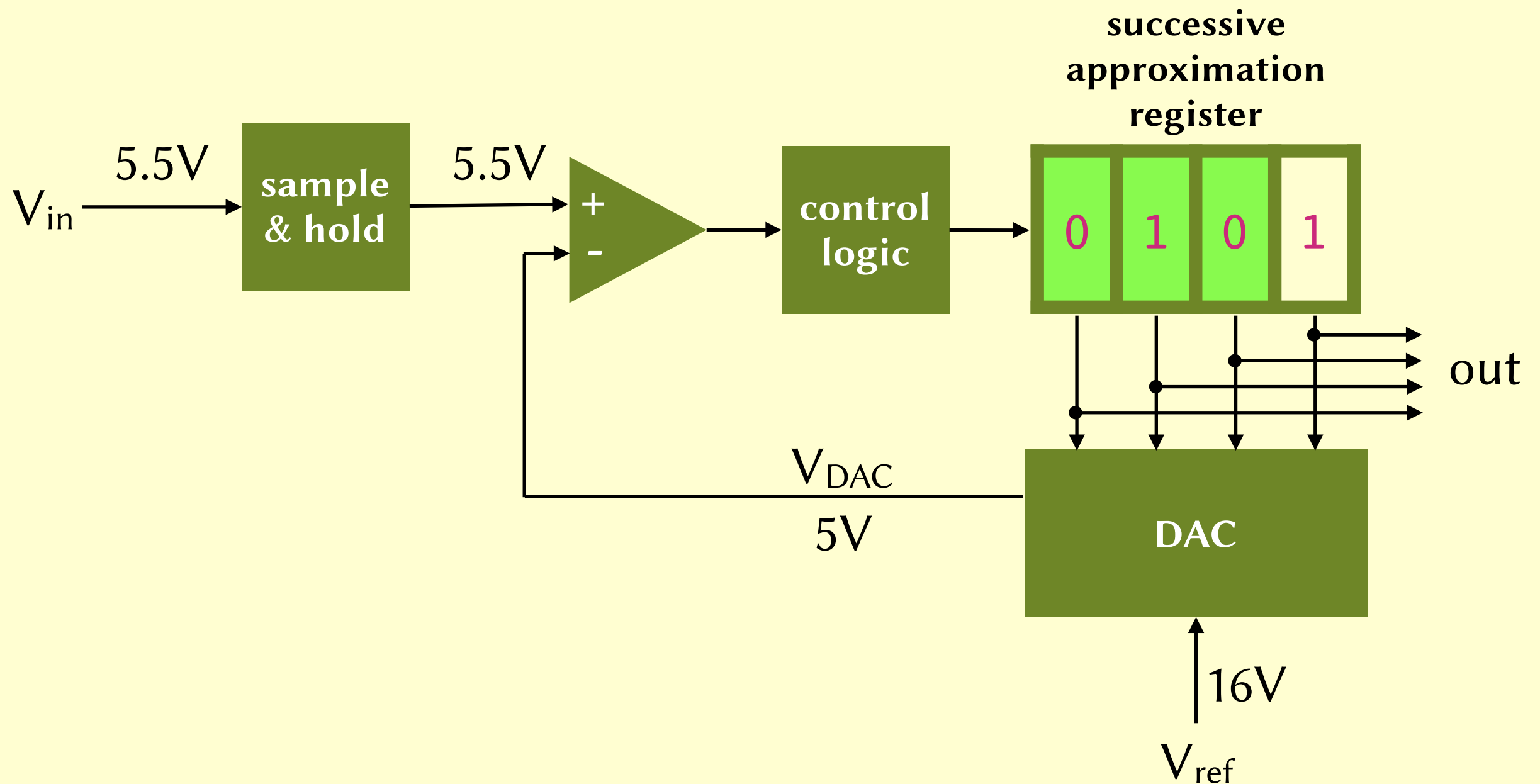

ADC using SAR

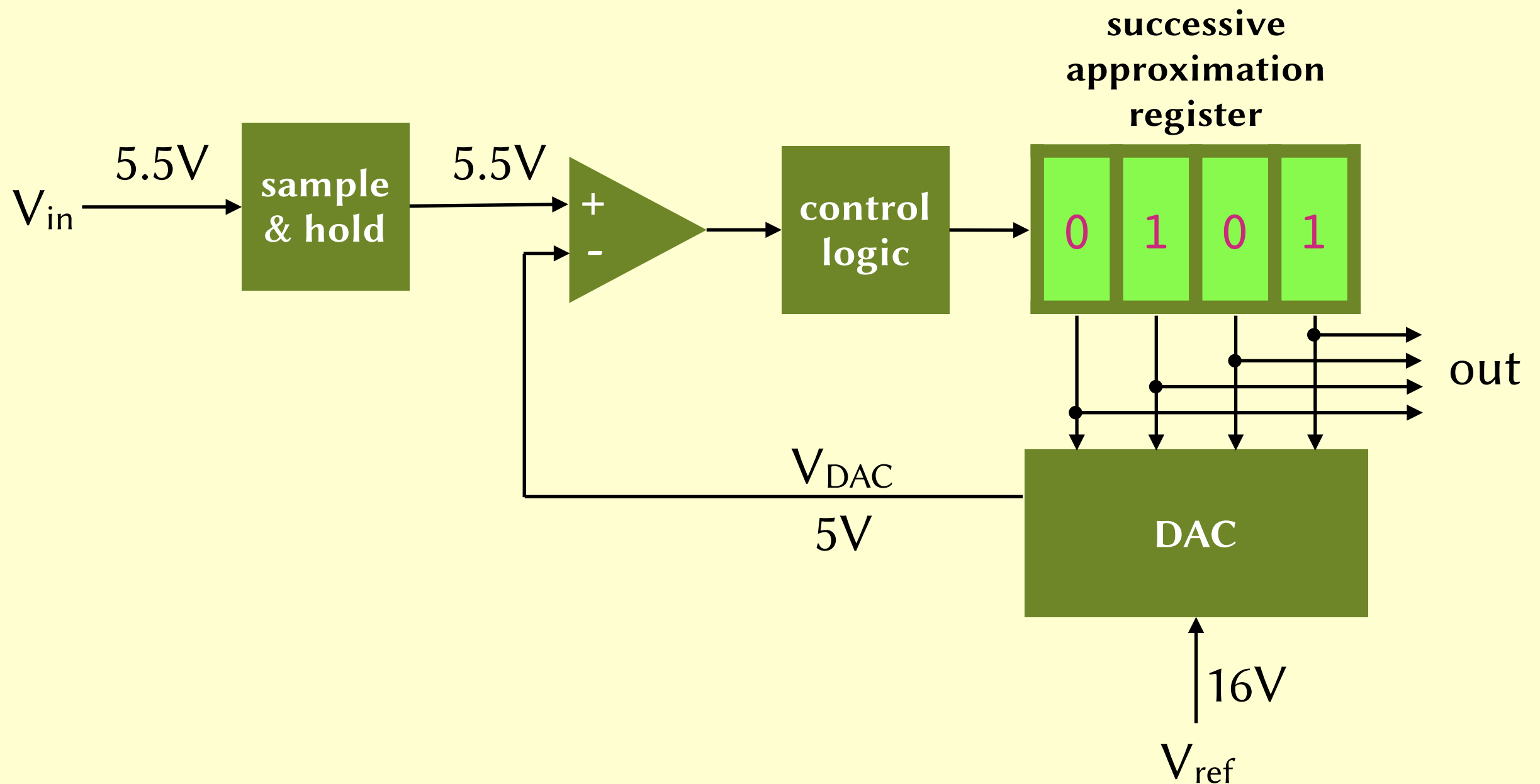

ADC using SAR

- An N-bit ADC takes N cycles to convert one sample
- Low power consumption
- Simple design with small circuit area
- Low latency
- More advanced designs are more efficient when the sampling rate is above 10MHz or $N > 16$.

This lecture


- The design of the spi2dac module
- How the ADC works
- **Wrapping up**

Module aims


- To ensure that all MSc students reach a **common competence level** in RTL design using FPGAs in a hardware description language.
- To act as a **revision exercise** for those already competent in Verilog and FPGAs.

Grading

 
- This lab is part of the Coursework component of the MSc course.
- You must pass this component, but it does not count towards your final MSc grade.



Coursework

 

Exams

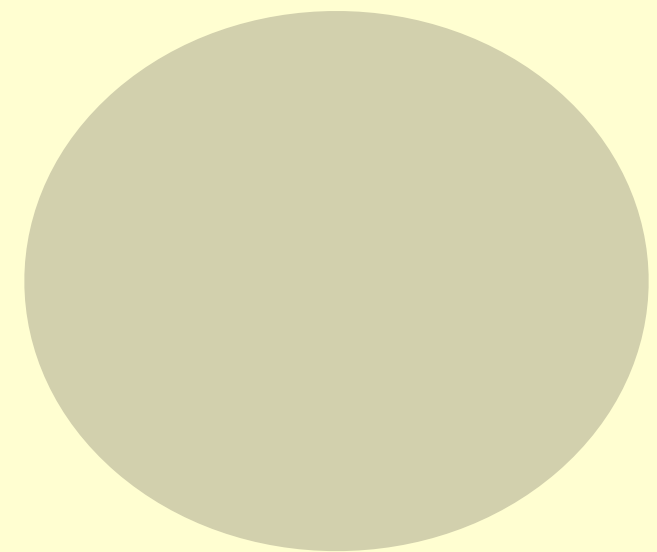

Project

Assessment

- Assessment will be via a 15-minute **oral interview**. This will assess:
 - how many parts of the experiment you have completed,
 - the extent to which you have understood the underlying principles of digital design, and
 - whether you have used a logbook (electronic or paper) to help you learn through planning and reflection.
- Please have your equipment set up and ready to demo.

Admin

- **Final lab:** Today at 1300–1600.
- **Teaching assistants:** Mr Jianyi Cheng and Mr He Li.

