

# Mastering Digital Design

with Verilog on FPGAs

John Wickerson

Lecture 3

# This lecture


- Pulse-width modulation (PWM)
- Finite state machines (FSMs)
- The analogue add-on card

# This lecture

- **Pulse-width modulation (PWM)**
- Finite state machines (FSMs)
- The analogue add-on card

 
# DAC via PWM

- **Digital-to-analogue conversion (DAC)** can be done using a network of resistors.
- It can also be done using digital components, via **pulse-width modulation (PWM)**.


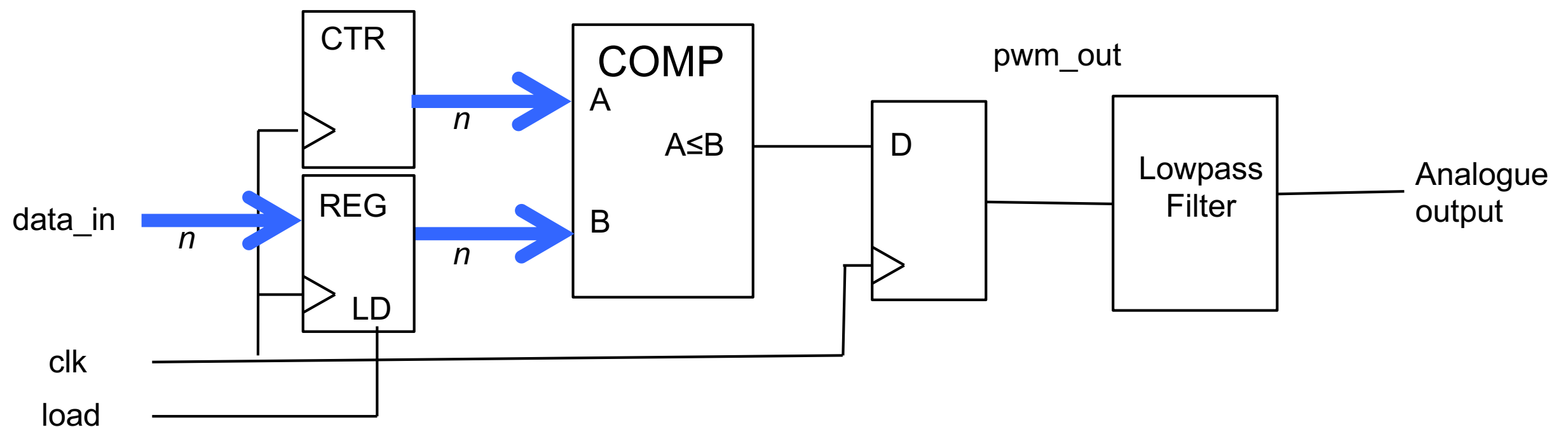
# DAC via PWM

- **Digital-to-analogue conversion (DAC)** can be done using a network of resistors.
- It can also be done using digital components, via **pulse-width modulation (PWM)**.



# DAC via PWM

```

module pwm (clk, data_in, load, pwm_out);
  input      clk;
  input [9:0] data_in;
  input      load;
  output     pwm_out;

  reg [9:0]  d;
  reg [9:0]  count;
  reg       pwm_out;

  initial count = 10'b0;

```


```

always @(posedge clk)
  if (load == 1'b1) d <= data_in;

always @(posedge clk) begin
  count <= count + 1'b1;

  if (count > d)
    pwm_out <= 1'b0;
  else
    pwm_out <= 1'b1;
  end
endmodule

```

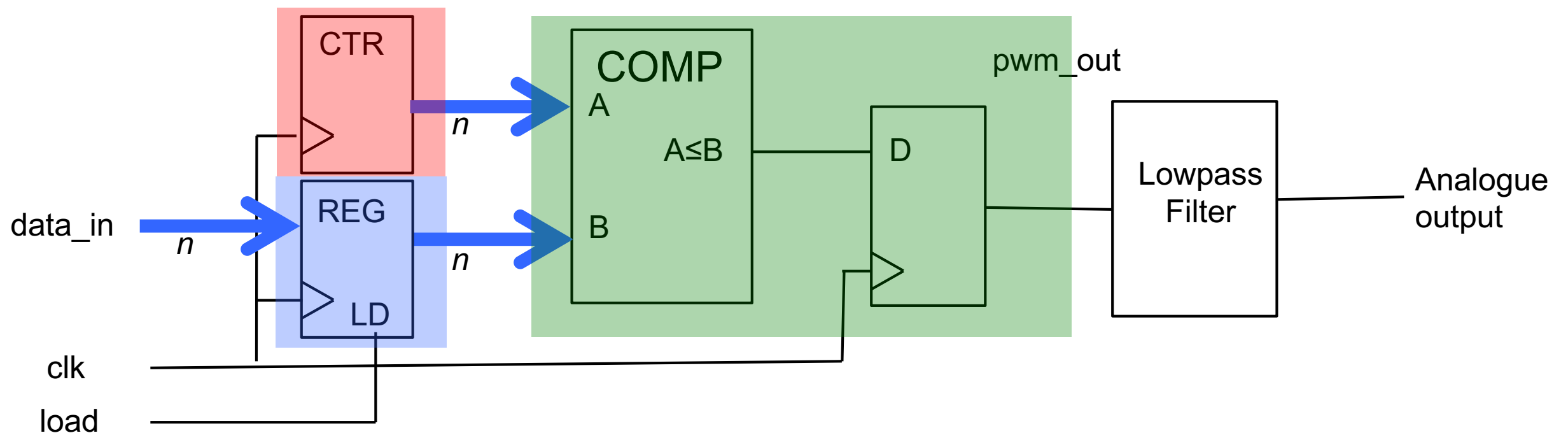

# This lecture

- Pulse-width modulation (PWM)
- Finite state machines (FSMs)
- The analogue add-on card



# This lecture

- Pulse-width modulation (PWM)
- **Finite state machines (FSMs)**
- The analogue add-on card




# Example 1: denoiser

- Task:

  


state	meaning	output
a	"definitely low"	0
b	"maybe rising"	0
c	"definitely high"	1
d	"maybe falling"	1

# Mealy machines

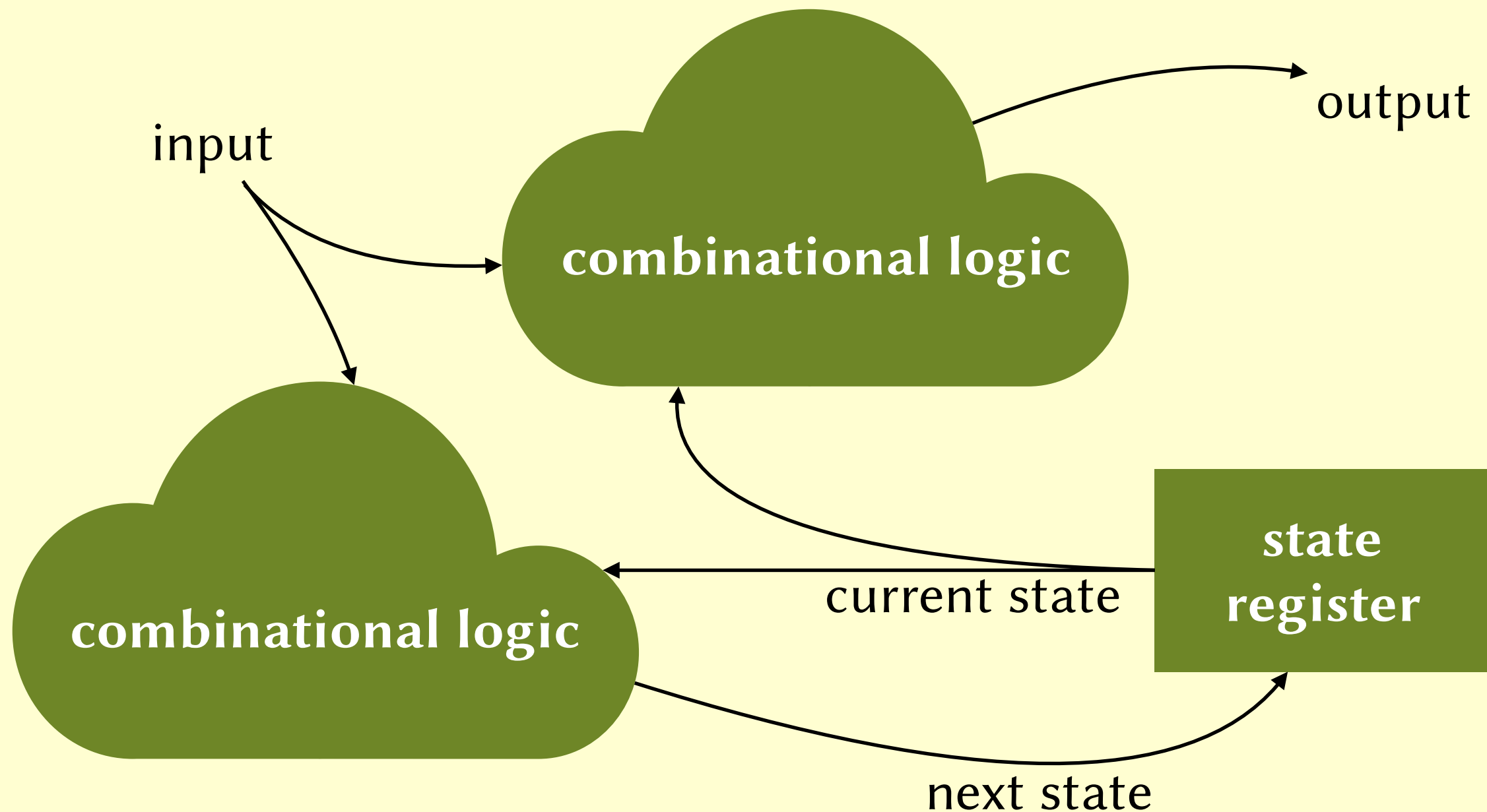

# Moore machines

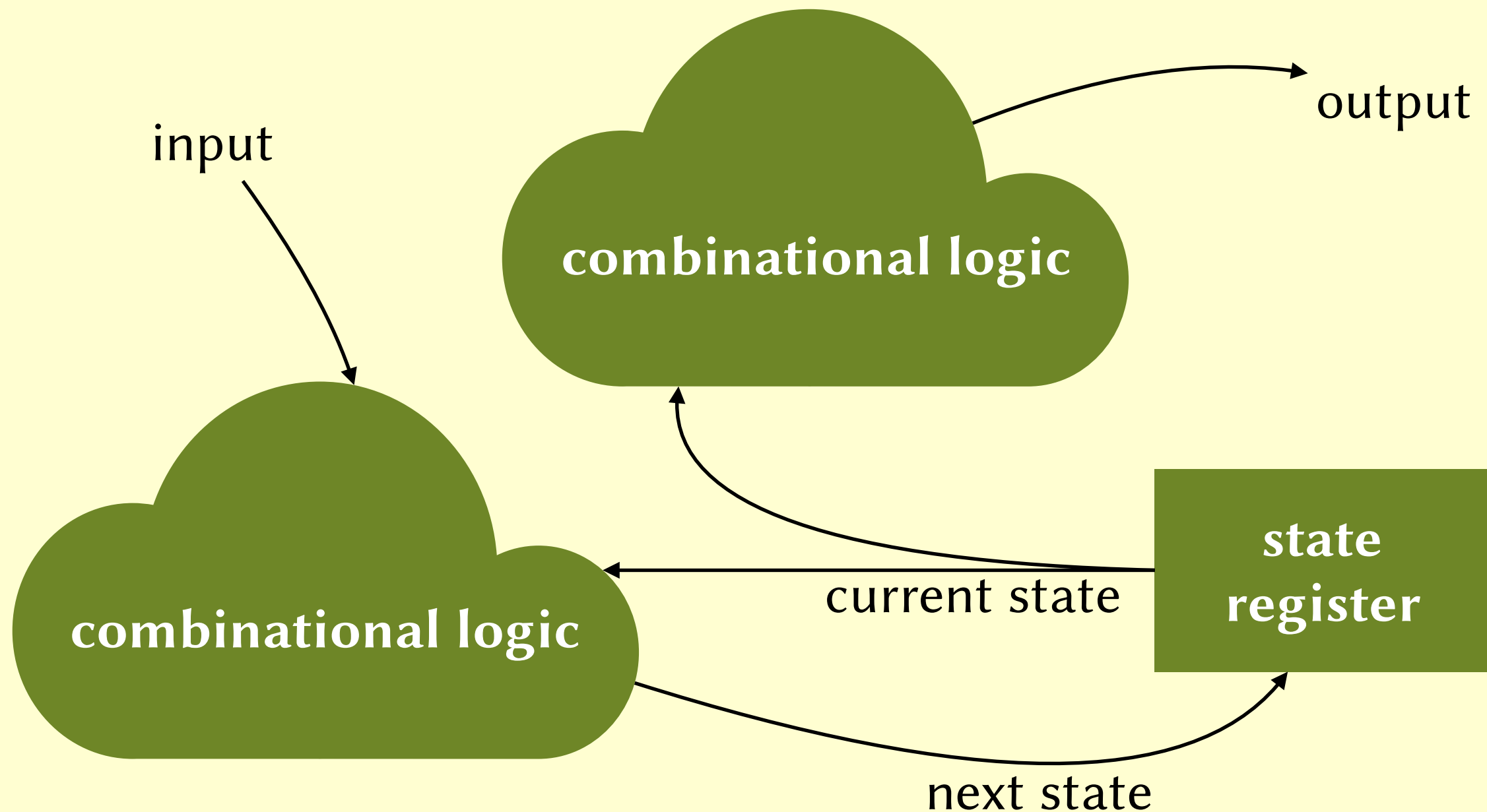

# Mealy vs Moore

- Mealy machines are a bit more complicated to design.
- Moore machines tend to require more states.
- Outputs of Moore machines are delayed.
- Named after George Mealy (1927–2010) and Edward Moore (1925–2003).




"Mealy Machine"  
developed in 1955  
by George H. Mealy



"Moore Machine"  
developed in 1956  
by Edward F. Moore


# Implementing the FSM

 

state	meaning	output
a	"definitely low"	0
b	"maybe rising"	0
c	"definitely high"	1
d	"maybe falling"	1

 
# Implementing the FSM

- Try to make the output value and the state number similar.
- Try to change one bit of the state number per transition.
- If two parts of the FSM have identical transitions, try to give the corresponding states similar numbers



state	meaning	output
00	"definitely low"	0
01	"maybe rising"	0
11	"definitely high"	1
10	"maybe falling"	1

# Implementing the FSM

 

state <i>s[1:0]</i>	meaning	output <i>out</i>	input <i>in</i>	next state <i>ns[1:0]</i>
00	"definitely low"	0	0	00
			1	01
01	"maybe rising"	0	0	00
			1	11
11	"definitely high"	1	0	10
			1	11
10	"maybe falling"	1	0	00
			1	11

# Implementing the FSM

```
assign out = s[1];
```

```
assign ns[1] = s[1] & s[0] | in & (s[0] | s[1]);
```

ns[1]	in=0	in=1
s=00	0	0
s=01	0	1
s=11	1	1
s=10	0	1

state s[1:0]	meaning	output out	input in	next state ns[1:0]
00	"definitely low"	0	0	00
			1	01
01	"maybe rising"	0	0	00
			1	11
11	"definitely high"	1	0	10
			1	11
10	"maybe falling"	1	0	00
			1	11



# Implementing the FSM


```
assign out = s[1];
```

```
assign ns[1] = s[1] & s[0] | in & (s[0] | s[1]);
```

```
assign ns[0] = in;
```

ns[0]	in=0	in=1
s=00	0	1
s=01	0	1
s=11	0	1
s=10	0	1

state s[1:0]	meaning	output out	input in	next state ns[1:0]
00	"definitely low"	0	0	00
			1	01
01	"maybe rising"	0	0	00
			1	11
11	"definitely high"	1	0	10
			1	11
10	"maybe falling"	1	0	00
			1	11

 

```
assign out = s[1];
assign ns[1] = s[1] & s[0] | in & (s[0] | s[1]);
assign ns[0] = in;
```

ns[0]	in=0	in=1
s=00	0	1
s=01	0	1
s=11	0	1
s=10	0	1

state s[1:0]	meaning	output out	input in	next state ns[1:0]
00	"definitely low"	0	0	00
			1	01
01	"maybe rising"	0	0	00
			1	11
11	"definitely high"	1	0	10
			1	11
10	"maybe falling"	1	0	00
			1	11

# One-hot encoding

- "One-hot" means "exactly one bit of a binary number is 1".

state	encoding as a binary number	one-hot encoding
a	00	0001
b	01	0010
c	11	0100
d	10	1000

- One-hot encoding uses more bits, but can lead to simpler logic.
- **Exercise.** Re-implement the FSM using one-hot encoding. Is the logic simpler?

# Automated FSM design


- We usually design FSMs at a higher level of abstraction.

declare  
states

calculate  
next state

```
module denoiser (out, in, clk, rst);
  input in, clk, rst; output out;
  parameter sA = 4'b0001;
  parameter sB = 4'b0010;
  parameter sC = 4'b0100;
  parameter sD = 4'b1000;
  reg [3:0] s; initial s = sA;
  reg out;      initial out = 1'b0;
```

 
```
  always @ (posedge clk)
    if (rst==1'b1) s <= sA;
    else case (s)
      sA: if (in==1'b1) s <= sB;
      sB: if (in==1'b1) s <= sC;
           else s <= sA;
      sC: if (in==1'b0) s <= sD;
      sD: if (in==1'b1) s <= sC;
           else s <= sA;
    endcase
```



```
  always @ *
    case (s)
      sA: out = 1'b0;
      sB: out = 1'b0;
      sC: out = 1'b1;
      sD: out = 1'b1;
    endcase
endmodule
```


calculate  
output

# The result

 


# Example 2: pulser

 - Task: Whenever the input rises, output a 1-cycle pulse.



# Example 2: pulser

declare  
states

 

```
module pulser (out, in, clk);  
  input in, clk; output out;  
  parameter SIDLE = 2'b00;  
  parameter SHIGH = 2'b01;  
  parameter SWAIT = 2'b10;  
  reg [1:0] s; initial s = SIDLE;  
  reg out;      initial out = 1'b0;
```

calculate  
next state





```
  always @ (posedge clk)  
    case (s)  
      SIDLE: if (in==1'b1) s <= SHIGH;  
      SHIGH: if (in==1'b1) s <= SWAIT;  
             else          s <= SIDLE;  
      SWAIT: if (in==1'b0) s <= SIDLE;  
    endcase
```

```
  always @ *  
    case (s)  
      SIDLE: out = 1'b0;  
      SHIGH: out = 1'b1;  
      SWAIT: out = 1'b0;  
    endcase  
endmodule
```

← calculate  
output

# Example 3: delayer

 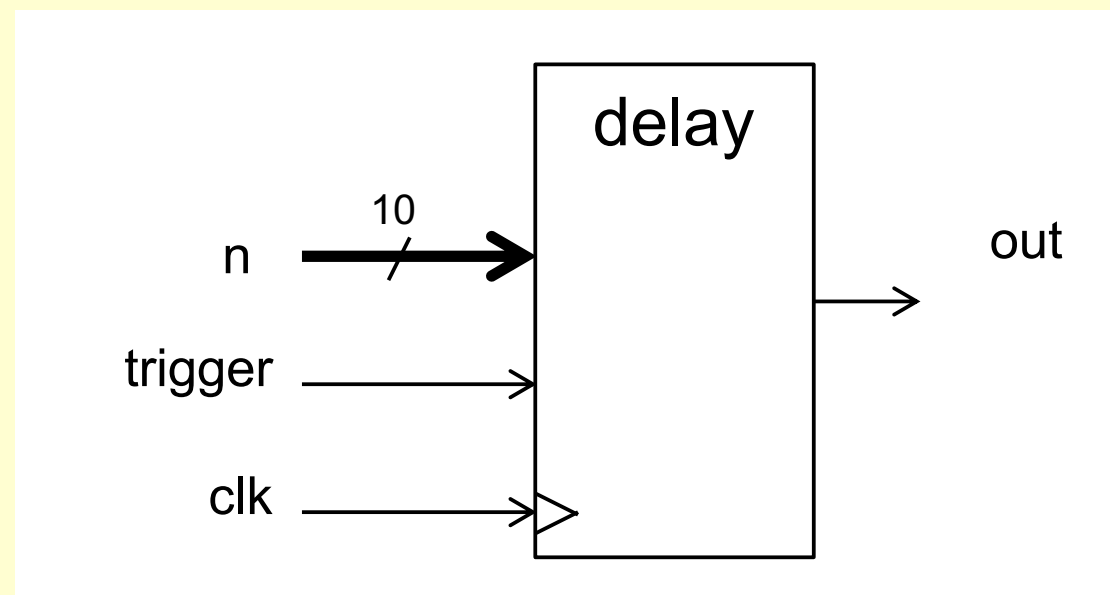- Task: when the 'trigger' input rises, wait for  $n$  cycles, then produce a 1-cycle pulse.






```

module delayer (out, in, n, clk);
  input in, clk; input [9:0] n; output out;
  parameter sIDLE = 2'b00;   parameter sDELA = 2'b01
  parameter sHIGH = 2'b11;   parameter sWAIT = 2'b10;
  reg [1:0] s; initial s = sIDLE;
  reg out;      initial out = 1'b0;
  reg [9:0] c;

  always @ (posedge clk)
    case (s) sIDLE: if (in==1'b1) s <= sDELA;
              sDELA: if (c==0) begin c <= n - 1'b1; s <= sHIGH; end
                  else                c <= c - 1'b1;
              sHIGH: if (in==1'b1) s <= sWAIT;
                  else                s <= sIDLE;
              sWAIT: if (in==1'b0) s <= sIDLE;
    endcase

  always @ *
    case (s) sIDLE: out = 1'b0;
              sDELA: out = 1'b0;
              sHIGH: out = 1'b1;
              sWAIT: out = 1'b0;
    endcase
endmodule

```

 

# This lecture


- Pulse-width modulation (PWM)
- Finite state machines (FSMs)
- The analogue add-on card

# This lecture


- Pulse-width modulation (PWM)
- Finite state machines (FSMs)
- **The analogue add-on card**
 
# The analogue I/O card

- Provides analogue inputs and outputs.
- Contains an ADC, a DAC, a low-pass filter, and an op-amp.
- Will be used for parts 3 and 4 of the experiment.




# Schematic

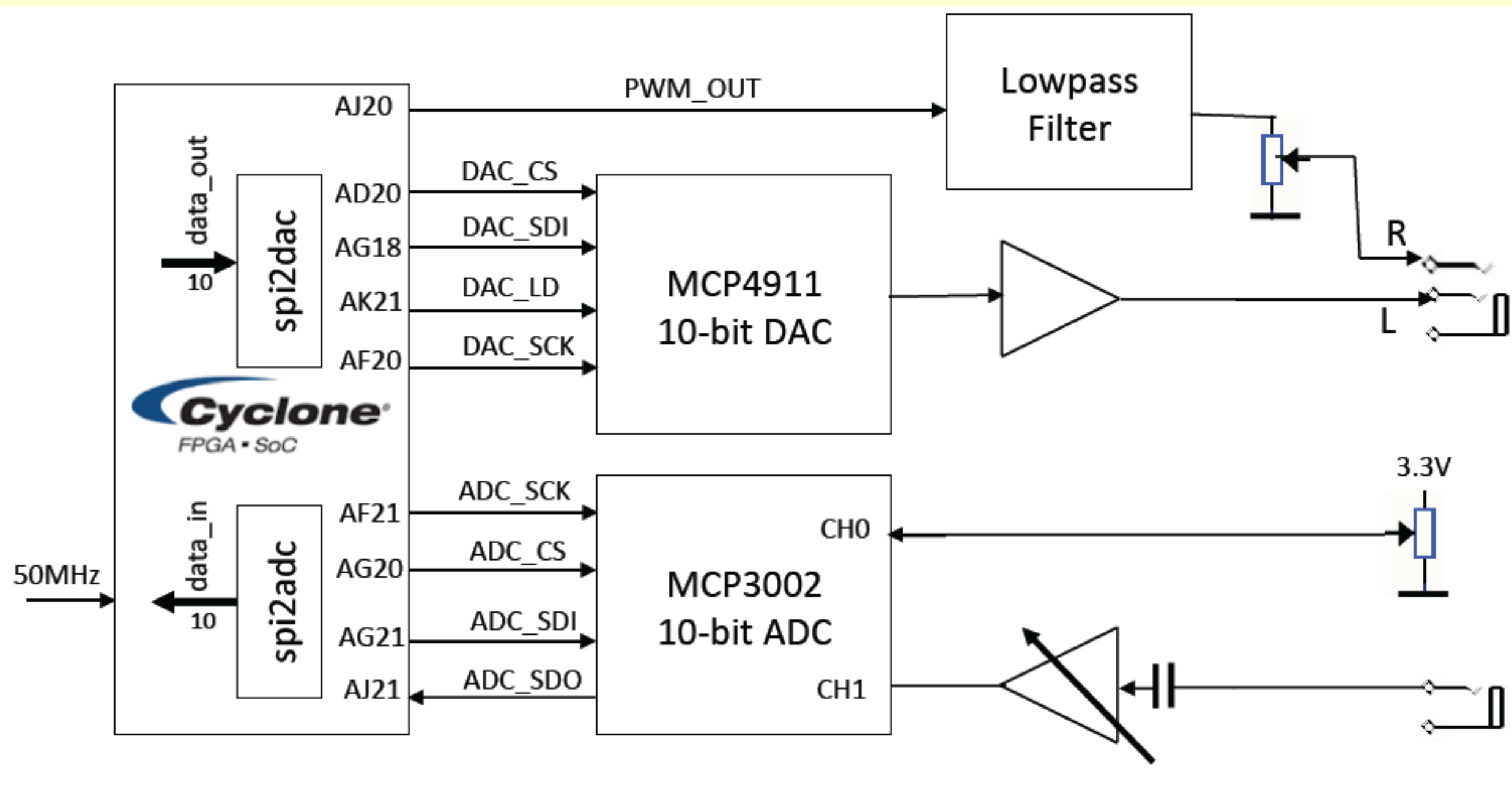
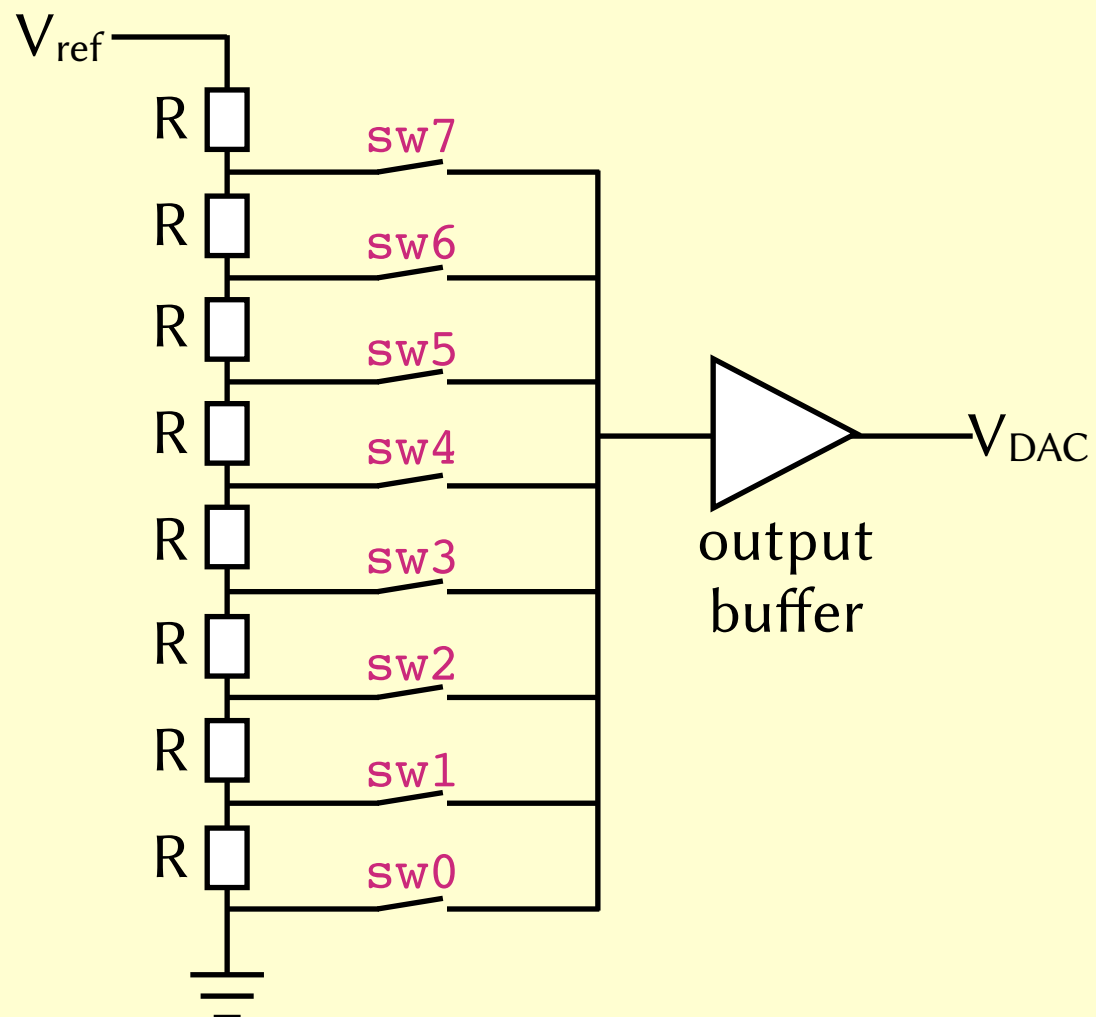
# DAC

- The DAC component uses a **resistor string** architecture




- Here is a 3-bit DAC. It uses  $2^3 = 8$  resistors. (The add-on card has a 10-bit DAC.)
- When the digital input is 5, we close (only) switch  $\text{sw5}$ , which means  $V_{\text{DAC}}$  is  $\frac{5}{8}V_{\text{ref}}$ .

# Series-parallel interface for DAC

- To send a value to the DAC, 16 bits are transmitted **serially**.
- **Chip select** (SC) going low means the start of transmission.
- Then **serial data in** (SDI) takes the following sequence of values.

bit	name	interpretation
15		always 0
14	BUF	whether $V_{\text{ref}}$ is buffered
13	$\neg$ GA	high = 1x gain, low = 2x gain
12	$\neg$ SHDN	high = normal, low = shutdown
11–2		the 10 bits of actual data
1–0		these are ignored

# spi2dac

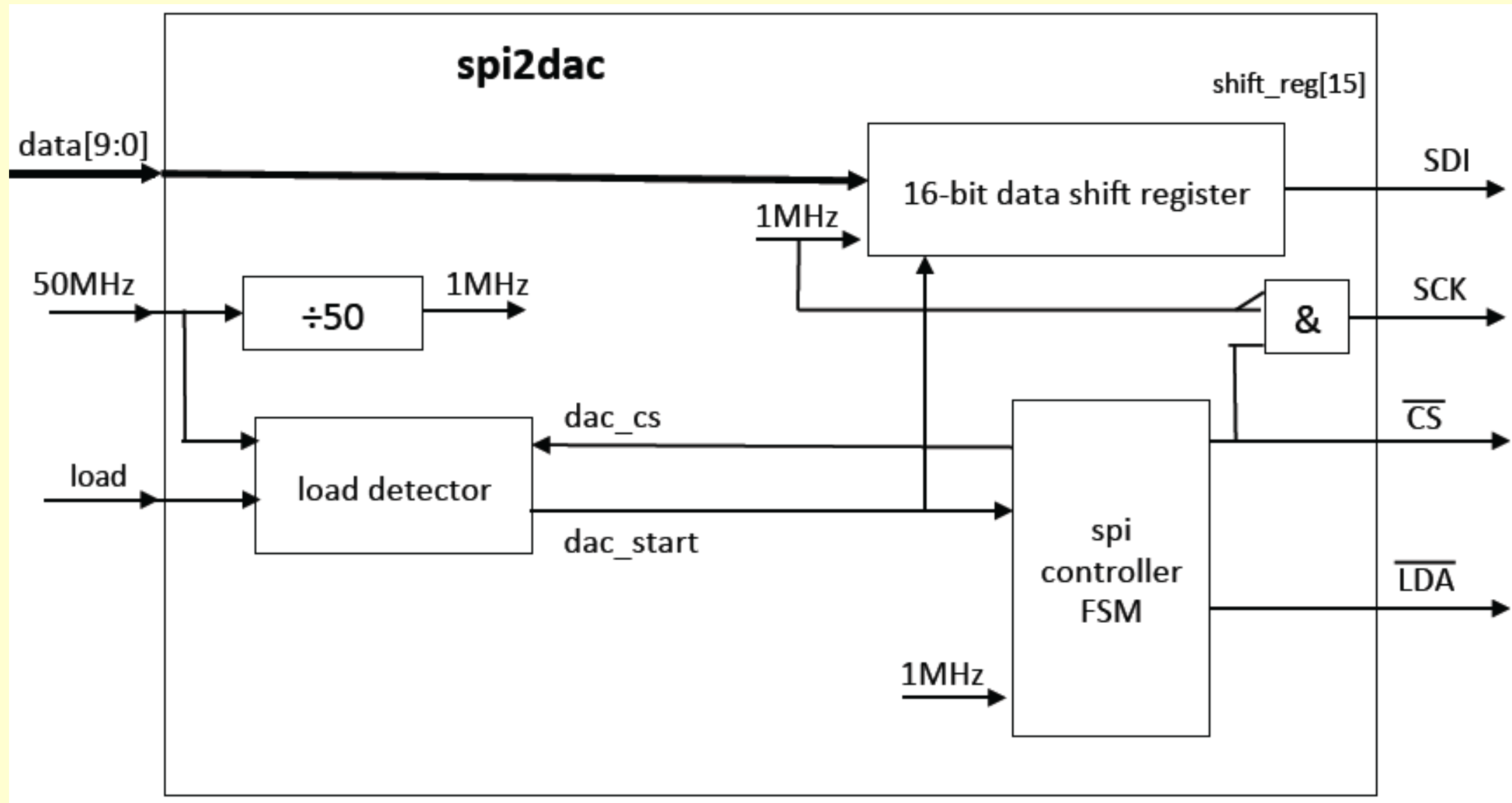

- More on this circuit next week!